 

Chapter Four

Arithmetic for Computers

Arithmetic

- **Where we've been:**
 - Performance (seconds, cycles, instructions)
 - Abstractions:
 - Instruction Set Architecture
 - Assembly Language and Machine Language
- **What's up ahead:**
 - Implementing the Architecture



Numbers

- **Bits are just bits (no inherent meaning)**
 - **conventions define relationship between bits and numbers**
- **Binary numbers (base 2)**
 - 0000 0001 0010 0011 0100 0101 0110 0111 1000 1001...**
 - decimal: $0 \dots 2^n - 1$**
- **Of course it gets more complicated:**
 - numbers are finite (overflow)**
 - fractions and real numbers**
 - negative numbers**
 - e.g., no MIPS subi instruction; addi can add a negative number)**
- **How do we represent negative numbers?**
 - i.e., which bit patterns will represent which numbers?**

Possible Representations

- | Sign Magnitude: | One's Complement | Two's Complement |
|-----------------|------------------|------------------|
| 000 = +0 | 000 = +0 | 000 = +0 |
| 001 = +1 | 001 = +1 | 001 = +1 |
| 010 = +2 | 010 = +2 | 010 = +2 |
| 011 = +3 | 011 = +3 | 011 = +3 |
| 100 = -0 | 100 = -3 | 100 = -4 |
| 101 = -1 | 101 = -2 | 101 = -3 |
| 110 = -2 | 110 = -1 | 110 = -2 |
| 111 = -3 | 111 = -0 | 111 = -1 |
- Issues: balance, number of zeros, ease of operations
- Which one is best? Why?

MIPS

- **32 bit signed numbers:**

0000	0000	0000	0000	0000	0000	0000	0000	$_{two}$	=	0_{ten}	
0000	0000	0000	0000	0000	0000	0000	0001	$_{two}$	=	$+ 1_{ten}$	
0000	0000	0000	0000	0000	0000	0000	0010	$_{two}$	=	$+ 2_{ten}$	
...											
0111	1111	1111	1111	1111	1111	1111	1110	$_{two}$	=	$+ 2,147,483,646_{ten}$	↙ <i>maxint</i>
0111	1111	1111	1111	1111	1111	1111	1111	$_{two}$	=	$+ 2,147,483,647_{ten}$	
1000	0000	0000	0000	0000	0000	0000	0000	$_{two}$	=	$- 2,147,483,648_{ten}$	↘ <i>minint</i>
1000	0000	0000	0000	0000	0000	0000	0001	$_{two}$	=	$- 2,147,483,647_{ten}$	
1000	0000	0000	0000	0000	0000	0000	0010	$_{two}$	=	$- 2,147,483,646_{ten}$	
...											
1111	1111	1111	1111	1111	1111	1111	1101	$_{two}$	=	$- 3_{ten}$	
1111	1111	1111	1111	1111	1111	1111	1110	$_{two}$	=	$- 2_{ten}$	
1111	1111	1111	1111	1111	1111	1111	1111	$_{two}$	=	$- 1_{ten}$	

Two's Complement Operations

- **Negating a two's complement number: invert all bits and add 1**
 - remember: “negate” and “invert” are quite different!
- **Converting n bit numbers into numbers with more than n bits:**
 - **MIPS 16 bit immediate gets converted to 32 bits for arithmetic**
 - **copy the most significant bit (the sign bit) into the other bits**
 - 0010 -> 0000 0010
 - 1010 -> 1111 1010
 - **"sign extension" (lbu vs. lb)**

Novas instruções

- instruções “unsigned”: (exemplo de aplicação, cálculo de memória)
- `sltu $t1, $t2, $t3` # diferença é “sem sinal”
- `slti` e `sltiu` # envolve imediato, com ou sem sinal

- Exemplo pag 215: `supor $s0 = FF FF FF FF` e `$s1 = 00 00 00 01`

`slt` `$t0, $s0, $s1`

como `$s0 < 0` e `$s1 > 0` \Rightarrow `$s0 < $s1` \Rightarrow `$t0 = 1`

`sltu` `$t0, $s0, $s1`

como `$s0` e `$s1` não tem sinal \Rightarrow `$s0 > $s1` \Rightarrow `$t0 = 0`

Cuidados com extensão 16 bits

- `beq $s0, $s1, nnn` # salta para PC + nnn se teste OK
- nnn tem 16 bits e PC tem 32 bits
 - estender de 16 para 32 bits antes da operação aritmética
- se `nnn > 0`
 - preencher com zeros à esquerda
- se `nnn < 0` CUIDADO
 - preencher com 1's à esquerda
 - verificar
- por este motivo operação é chamada de
 - **EXTENSÃO DE SINAL**

Addition & Subtraction

- Just like in grade school (carry/borrow 1s)

$$\begin{array}{r} 0111 \\ + 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0111 \\ - 0110 \\ \hline \end{array} \qquad \begin{array}{r} 0110 \\ - 0101 \\ \hline \end{array}$$

- Two's complement operations easy
 - subtraction using addition of negative numbers

$$\begin{array}{r} 0111 \\ + 1010 \\ \hline \end{array}$$

- Overflow (result too large for finite computer word):
 - e.g., adding two n-bit numbers does not yield an n-bit number

$$\begin{array}{r} 0111 \\ + 0001 \\ \hline \underline{\quad} 1000 \end{array} \quad \textit{note that overflow term is somewhat misleading, it does not mean a carry "overflowed"}$$

Detecting Overflow

- No overflow when adding a positive and a negative number
- No overflow when signs are the same for subtraction
- **CONDIÇÕES DE OVERFLOW**

op	A	B	resultado
A+B	+	+	-
A+B	-	-	+
A-B	+	-	-
A-B	-	+	+

Em hardware, comparar o “vai-um” e o “vem-um” com relação ao bit de sinal

Effects of Overflow

- **An exception (interrupt) occurs**
 - **Control jumps to predefined address for exception (EPC — EXCEPTION PROGRAM COUNTER)**
 - **Interrupted address is saved for possible resumption**
 - **mfc0 (move from system control): copia endereço do EPC para qualquer registrador**
- **Don't always want to detect overflow**
 - **new MIPS instructions: addu, addiu, subu**

note: addiu still sign-extends!

note: sltu, sltiu for unsigned comparisons

Instruções (fig 4.52 - pag 309)

add	add	R
add immediate	addi	I
add unsigned	addu	R
add immediate unsigned	addiu	I
subtract	sub	R
subtract unsigned	subu	R
and	and	R
and immediate	andi	I
or	or	R
or immediate	ori	I
shift left logical	sll	R
shift right logical	srl	R
load upper immediate	lui	I
load word	lw	I
store word	sw	I
load byte unsigned	lbu	I
store byte	sb	I
branch on equal	beq	I
branch on not equal	bne	I
jump	j	J
jump and link	jal	J
jump register	jr	R
set less than	slt	R
set less than immediate	slti	I
set less than unsigned	sltu	R
set less than immediate unsigned	sltiu	I

multiply	mult	R
multiply unsigned	multu	R
divide	div	R
divide unsigned	divu	R
move from Hi	mfhi	R
move from Lo	mflo	R
move from system control (EPC)	mfc0	R
fp add single	add.s	R
fp add double	add.d	R
fp subtract single	sub.s	R
fp subtract double	sub.d	R
fp multiply single	mul.s	R
fp multiply double	mul.d	R
fp divide single	div.s	R
fp divide double	div.d	R
load word to fp single	lwc1	I
store word to fp single	swc1	I
branch on fp true	bclt	I
branch on fp false	bclf	I
fp compare single (x= eq, neq, lt, le, gt, ge)	c.x.s	R
fp compare double (x= eq, neq, lt, le, gt, ge)	c.x.d	R

Review: Boolean Algebra & Gates

- **Problem: Consider a logic function with three inputs: A, B, and C.**

Output D is true if at least one input is true



Output E is true if exactly two inputs are true

Output F is true only if all three inputs are true


- **Show the truth table for these three functions.**
- **Show the Boolean equations for these three functions.**
- **Show an implementation consisting of inverters, AND, and OR gates.**

An ALU (arithmetic logic unit)

  - Let's build an ALU to support the `andi` and `ori` instructions
 - we'll just build a 1 bit ALU, and use 32 of them




 - Possible Implementation (sum-of-products):



Review: The Multiplexor

 - Selects one of the inputs to be the output, based on a control input




*note: we call this a 2-input mux
even though it has 3 inputs!*

- Lets build our ALU using a MUX:

Different Implementations


 
- Not easy to decide the “best” way to build something
 - Don't want too many inputs to a single gate
 - Dont want to have to go through too many gates
 - for our purposes, ease of comprehension is important
- Let's look at a 1-bit ALU for addition:



$$c_{out} = a b + a c_{in} + b c_{in}$$
$$sum = a \text{ xor } b \text{ xor } c_{in}$$

- How could we build a 1-bit ALU for add, and, and or?
- How could we build a 32-bit ALU?

Building a 32 bit ALU

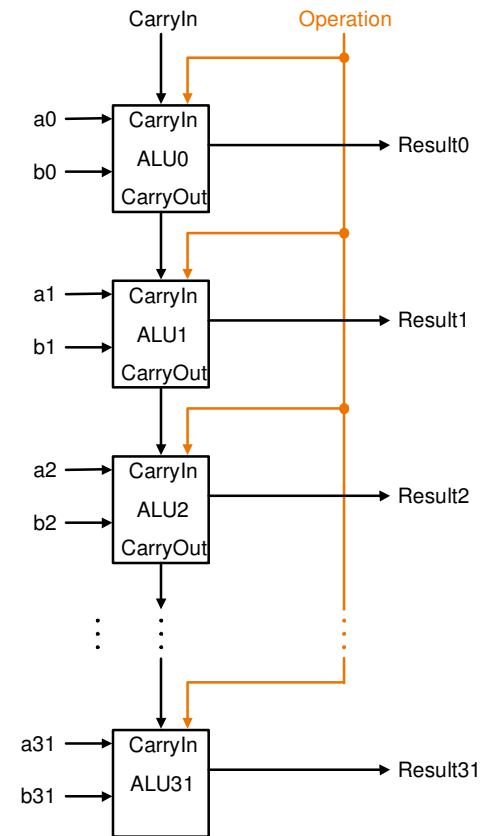 

What about subtraction (a - b) ?


- Two's complement approach: just negate b and add.

$$a - b = a + (-b)$$


- How do we negate?

$$(-a) = \text{comp}_2(a) = \text{comp}_1(a) + 1$$



- A very clever solution:

 

Subtrator

 

equivalente à

 
 


Tailoring the ALU to the MIPS


- **Need to support the set-on-less-than instruction (slt)**
 - remember: **slt** is an arithmetic instruction
 - produces a **1** if $rs < rt$ and **0** otherwise
 - use subtraction: $(a-b) < 0$ implies $a < b$
- **Need to support test for equality (beq \$t5, \$t6, \$t7)**
 - use subtraction: $(a-b) = 0$ implies $a = b$

Supporting slt


- Can we figure out the idea?

  

a.

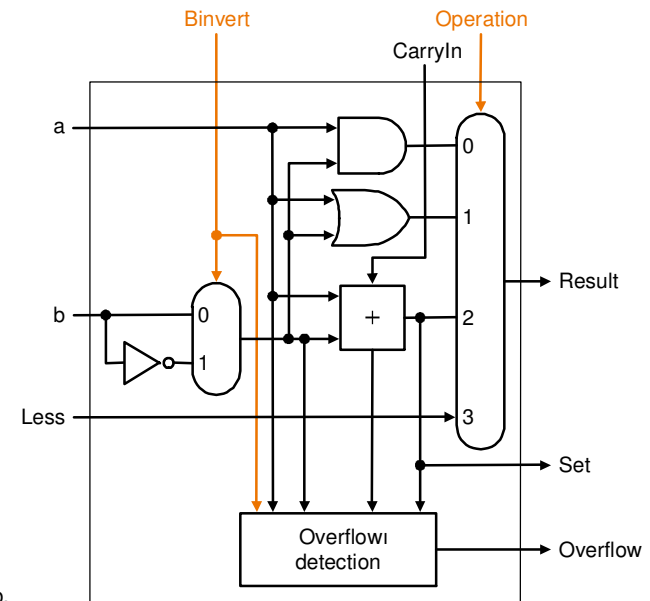

b.

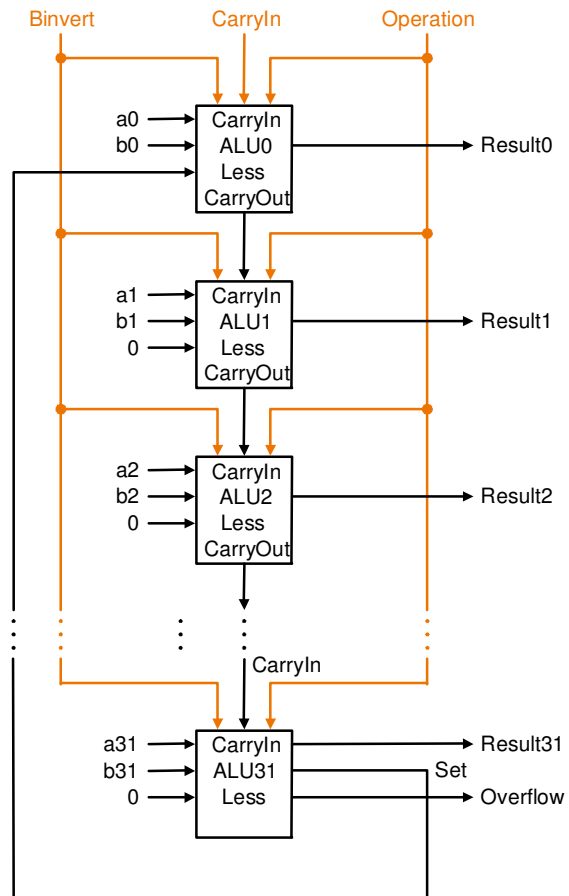


Test for equality


- Notice control lines:

000 = and
001 = or
010 = add
110 = subtract
111 = slt

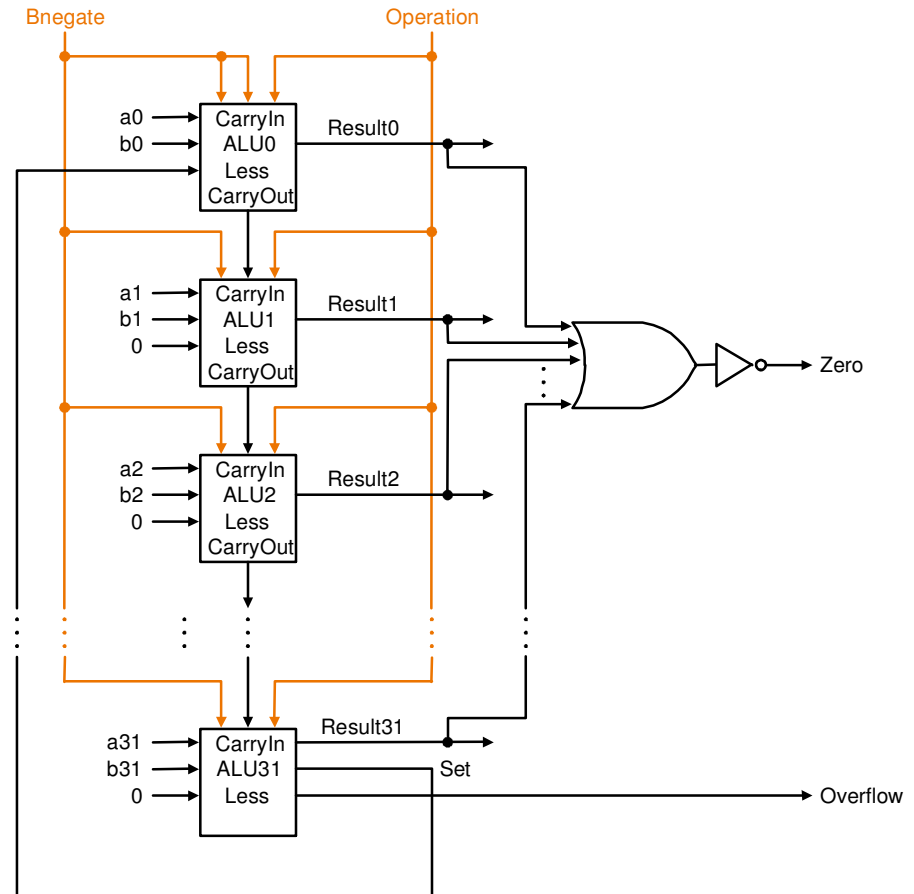•*Note: zero is a 1 when the result is zero!*



ALU

 

32 bits: A, B, result

1 bit: Zero, Overflow

3 bits: ALUop

ALUop Binv-OP	Instrução
0 00	and
0 01	or
0 10	add
1 10	sub
1 11	slt
1 10	beq

Conclusion

- **We can build an ALU to support the MIPS instruction set**
 - key idea: use multiplexor to select the output we want
 - we can efficiently perform subtraction using two's complement
 - we can replicate a 1-bit ALU to produce a 32-bit ALU
- **Important points about hardware**
 - all of the gates are always working
 - the speed of a gate is affected by the number of inputs to the gate
 - the speed of a circuit is affected by the number of gates in series (on the “critical path” or the “deepest level of logic”)
- **Our primary focus: comprehension, however,**
 - Clever changes to organization can improve performance (similar to using better algorithms in software)
 - we'll look at two examples for addition and multiplication

Problem: ripple carry adder is slow

- Is a 32-bit ALU as fast as a 1-bit ALU?
atraso (ent \Rightarrow soma ou carry = $2G$)
n estágios $\Rightarrow 2nG$
- Is there more than one way to do addition?
 - two extremes:
ripple carry ($2nG$)
sum-of-products ($2G$)

Can you see the ripple? How could you get rid of it?

$$c_1 = b_0c_0 + a_0c_0 + a_0b_0$$

$$c_2 = b_1c_1 + a_1c_1 + a_1b_1$$

$$c_3 = b_2c_2 + a_2c_2 + a_2b_2$$


$$c_4 = b_3c_3 + a_3c_3 + a_3b_3$$

$$c_2 =$$

$$c_3 =$$

$$c_4 =$$

Not feasible! Why?

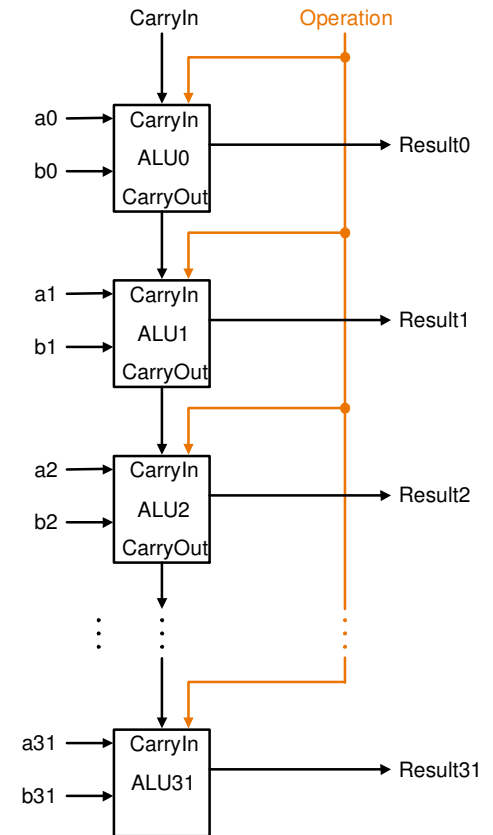

Carry-lookahead adder

- An approach in-between our two extremes
- Motivation:
 - If we didn't know the value of carry-in, what could we do?
 - When would we always generate a carry? $g_i = a_i b_i$
 - When would we propagate the carry? $p_i = a_i + b_i$
- Did we get rid of the ripple?

$$c_1 = g_0 + p_0 c_0$$

$$c_2 = g_1 + p_1 c_1 \quad c_2 =$$

$$c_3 = g_2 + p_2 c_2 \quad c_3 =$$


$$c_4 = g_3 + p_3 c_3 \quad c_4 =$$

Feasible! Why?

- atraso: ent $\Rightarrow g_i p_i$ (1G)
 - $g_i p_i \Rightarrow$ carry (2G)
 - carry \Rightarrow saídas (2G)

total: 5G independente de n

Use principle to build bigger adders

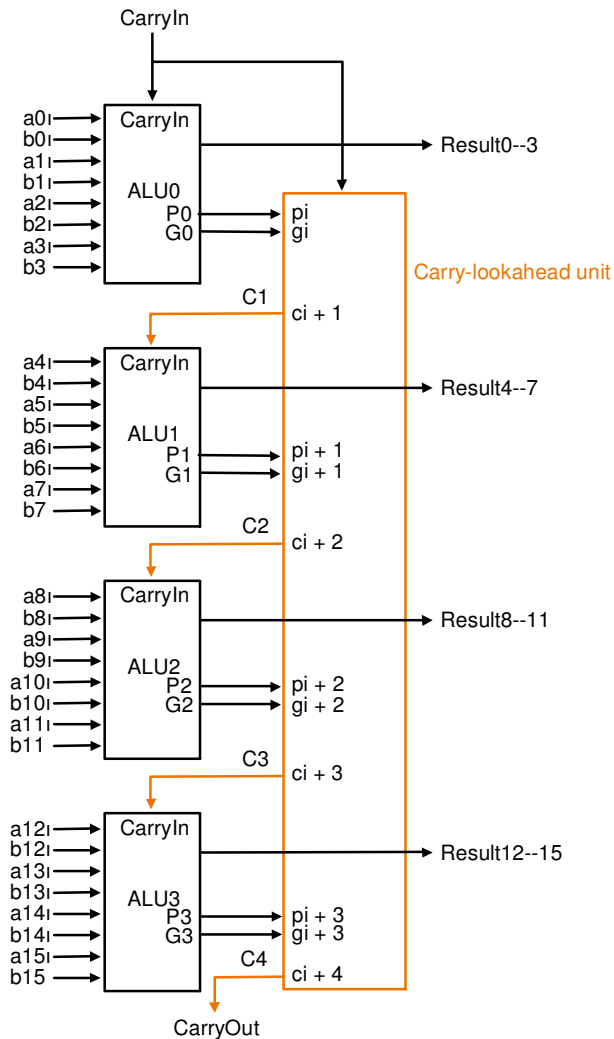

- **Can't build a 16 bit adder this way... (too big)**
- **Could use ripple carry of 4-bit CLA adders**
- **Better: use the CLA principle again!**
 - **super propagate (ver pag 243)**
 - **super generate (ver pag 245)**
 - **ver exercícios 4.44, 45 e 46 (não será cobrado)**

Multiplication



- **More complicated than addition**
 - accomplished via shifting and addition
- **More time and more area**
- **Let's look at 3 versions based on gradeschool algorithm**

$$\begin{array}{r}
 8_{10} \quad 1000 \text{ multiplicando} \\
 9_{10} \quad 1001 \text{ multiplicador} \\
 \hline
 \quad 1000 \\
 \quad 0000 \\
 \quad 0000 \text{ produtos parciais} \\
 \quad 1000 \\
 \hline
 72_{10} \quad 1001000
 \end{array}$$


$\max = (2^4 - 1) * (2^4 - 1) = 225$
 $225 > 128 \Rightarrow 8 \text{ bits}$
 $32 * 32 \text{ bits} \Rightarrow 64 \text{ bits}$

- **Negative numbers: convert and multiply**
 - there are better techniques, we won't look at them



Multiplication: Implementation

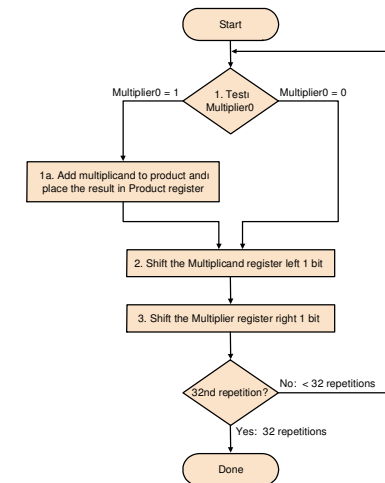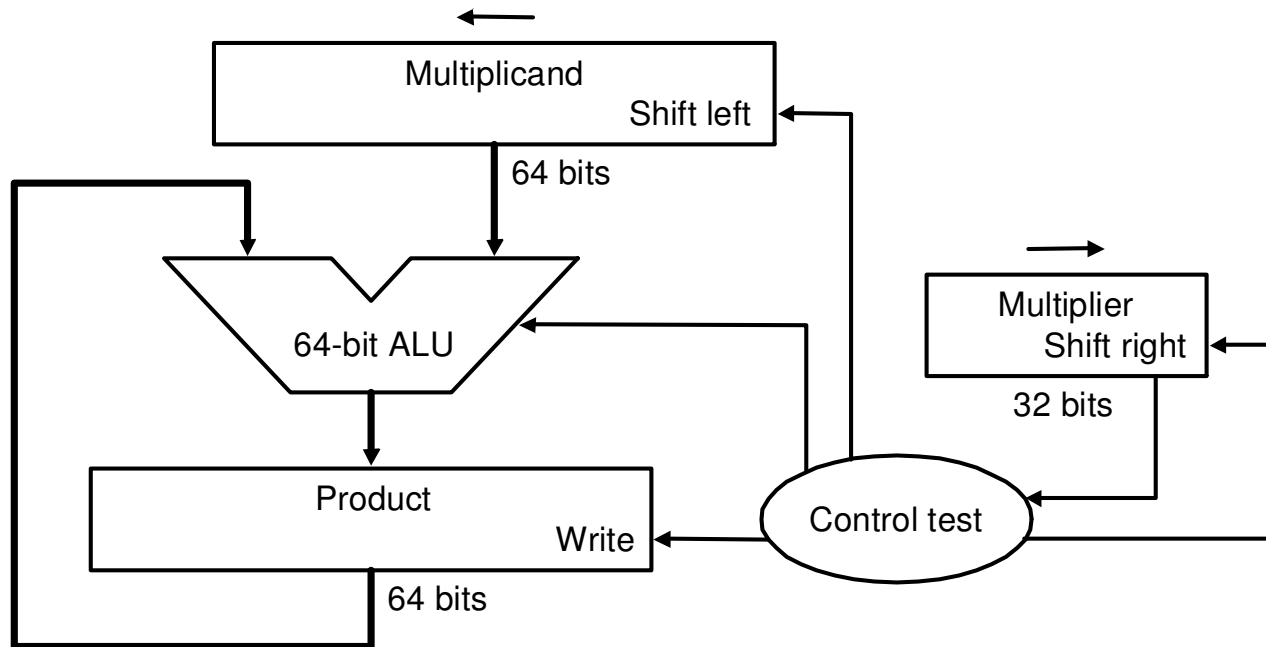

Second Version

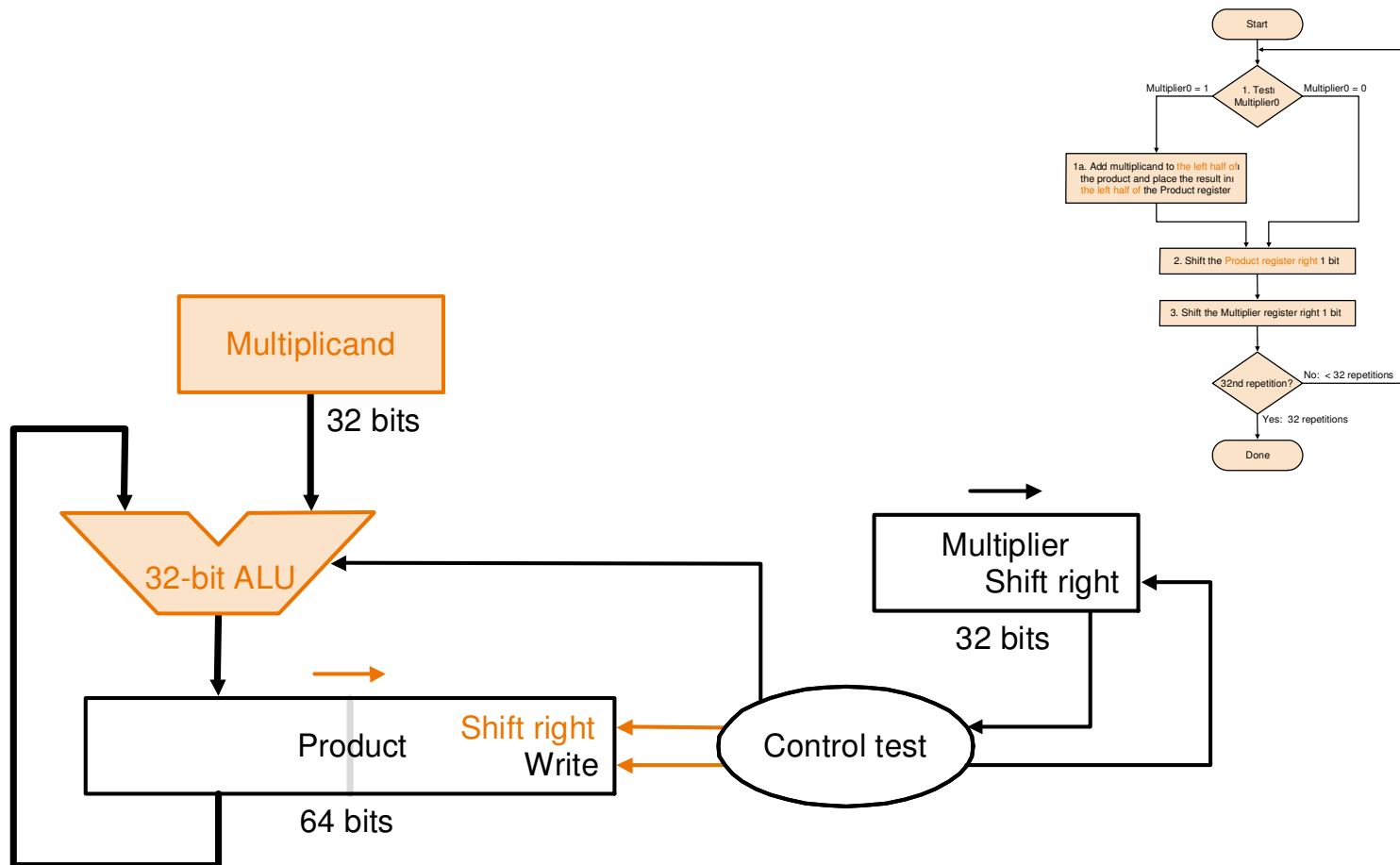

Final Version

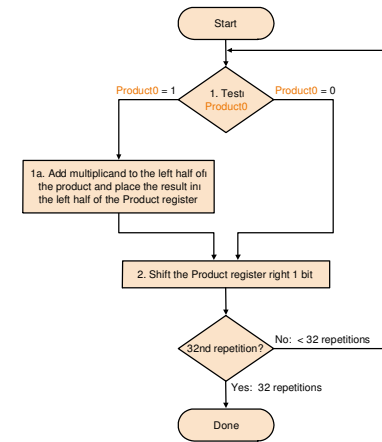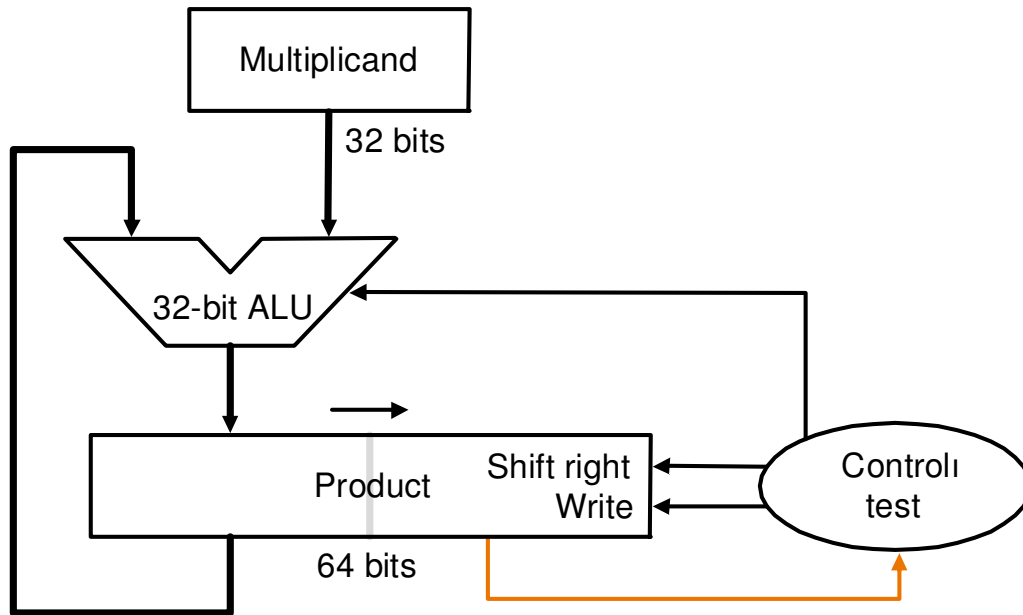

- **No MIPS:**

- dois novos registradores de uso dedicado para multiplicação: Hi e Lo (32 bits cada)

- **mult \$t1, \$t2** # Hi Lo \leftarrow \$t1 * \$t2

- **mfhi \$t1** # \$t1 \leftarrow Hi

- **mflo \$t1** # \$t1 \leftarrow Lo

Algoritmo de Booth (visão geral)


- **Idéia: “acelerar” multiplicação no caso de cadeia de “1’s” no multiplicador:**

$$\begin{array}{r} 0\ 1\ 1\ 1\ 0\ * \text{ (multiplicando)} = \\ +\ 1\ 0\ 0\ 0\ 0\ * \text{ (multiplicando)} \\ -\ 0\ 0\ 0\ 1\ 0\ * \text{ (multiplicando)} \end{array}$$





- **Olhando bits do multiplicador 2 a 2**
 - 00 nada
 - 01 soma (final)
 - 10 subtrai (começo)
 - 11 nada (meio da cadeia de uns)
- **Funciona também para números negativos**
- **Para o curso: só os conceitos básicos**
- **Algoritmo de Booth estendido**
 - varre os bits do multiplicador de 2 em 2
- **Vantagens:**
 - (pensava-se: shift é mais rápido do que soma)
 - gera metade dos produtos parciais: metade dos ciclos

Geração rápida dos produtos parciais

	Y_0	Y_1	Y_2
	X_0	X_1	X_2
	$X_2 Y_0$	$X_2 Y_1$	$X_2 Y_2$
	$X_1 Y_0$	$X_1 Y_1$	$X_1 Y_2$
	$X_0 Y_0$	$X_0 Y_1$	$X_0 Y_2$

 

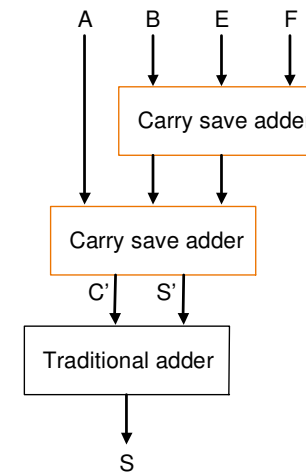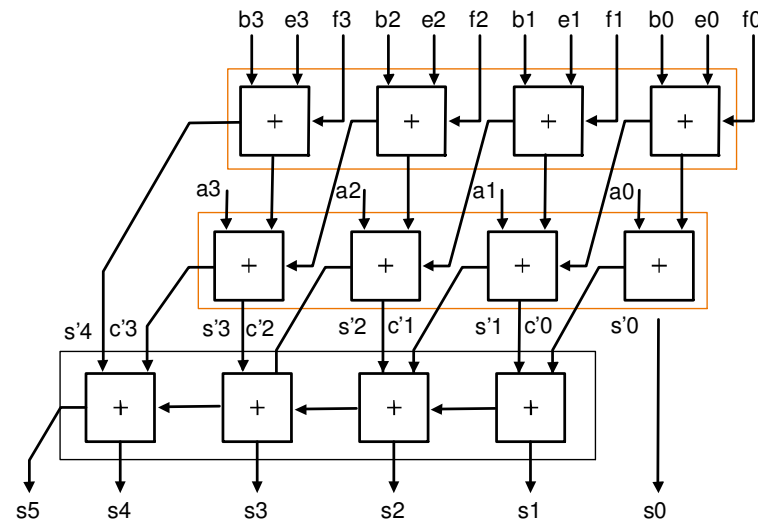 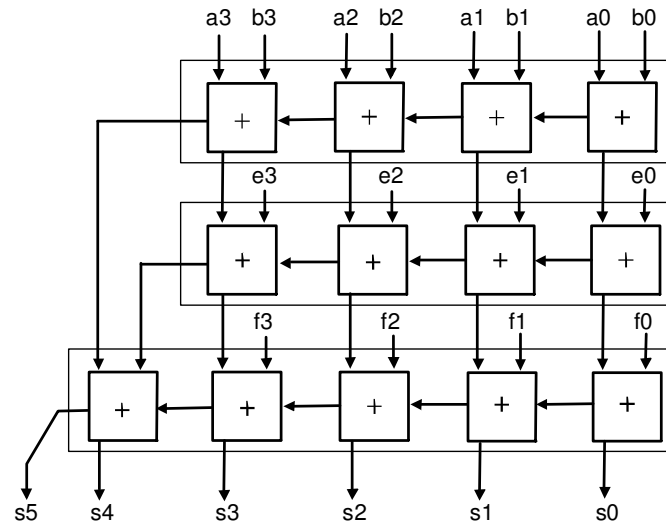Carry Save Adders (soma de produtos parciais)



Divisão

$$29 \div 3 \Rightarrow 29 = 3 * Q + R = 3 * 9 + 2$$

dividendo
divisor
quociente
resto

$$29_{10} = 011101 \quad 3_{10} = 11$$

$\begin{array}{r} 011101 \\ \underline{11} \\ 00101 \\ \underline{11} \\ 10 \end{array}$	$\begin{array}{r} 11 \\ \hline 01001 \end{array}$	$Q = 9 \quad R = 2$
--	---	---------------------

Como implementar em hardware?

Alternativa 1: divisão com restauração

- hardware não sabe se “vai caber ou não”
- registrador para guardar resto parcial
- verificação do sinal do resto parcial
- caso negativo \Rightarrow restauração

$29 - 3 * 2^4 = -19$	$q_4 = 1$	
$-19 + 3 * 2^4 = 29$	$q_4 = 0$	Restauração
<hr/>		
$29 - 3 * 2^3 = 5$	$q_3 = 1$	
<hr/>		
$5 - 3 * 2^2 = -7$	$q_2 = 1$	
$-7 + 3 * 2^2 = 5$	$q_2 = 0$	Restauração
<hr/>		
$5 - 3 * 2^1 = -1$	$q_1 = 1$	
$-1 + 3 * 2^1 = 5$	$q_1 = 0$	Restauração
<hr/>		
$5 - 3 * 2^0 = 2$	$q_0 = 1$	

$$R = 11 = 2 \quad q_4 q_3 q_2 q_1 q_0 = 01001 = 9$$

Alternativa 2: divisão sem restauração

Regras

se resto parcial	> 0	próxima operação	soma	objetivo R → 0
se resto parcial	< 0	próxima operação	subtração	

se operação corrente	+	$q_i = \neq$
se operação corrente	-	$q_i = 1$

$29 - 3 * 2^4 = -19 < 0$	próx = SOMA	$q_4 = 1$
$-19 + 3 * 2^3 = 5 > 0$	próx = SUB	$q_3 = \neq$
$5 - 3 * 2^2 = -7 < 0$	próx = SOMA	$q_2 = 1$
$-7 + 3 * 2^1 = -1 < 0$	próx = SOMA	$q_1 = \neq$
$-1 + 3 * 2^0 = 2$		$q_0 = \neq$

Resto = 2

Quociente = ~~1111~~ ??

Alternativa 2: conversão do resultado

$$1 \bar{1} 1 \bar{1} \bar{1} = (2^4 - 2^3 + 2^2 - 2^1 - 2^0)$$

$$16 - 8 + 4 - 2 - 1$$

$$\dots 1 \bar{1} \dots = 2^n - 2^{(n-1)} = 2^{(n-1)}(2 - 1) = 2^{(n-1)}$$


$$1 \bar{1} 1 \bar{1} \bar{1}$$

$$0 1 0 1 \bar{1}$$



$$0 1$$

- N° de somas: 3
- N° de subtrações: 2
- Total: 5
- OBS: se resto < 0 deve haver correção de um divisor para que resto > 0

Comparação das alternativas

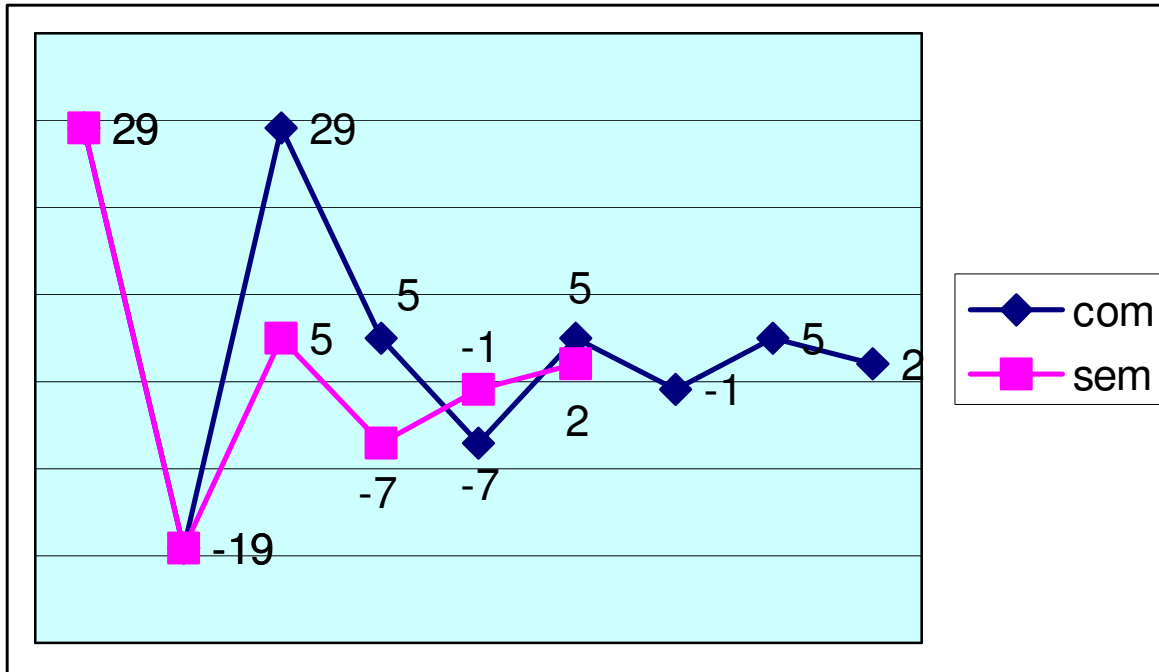

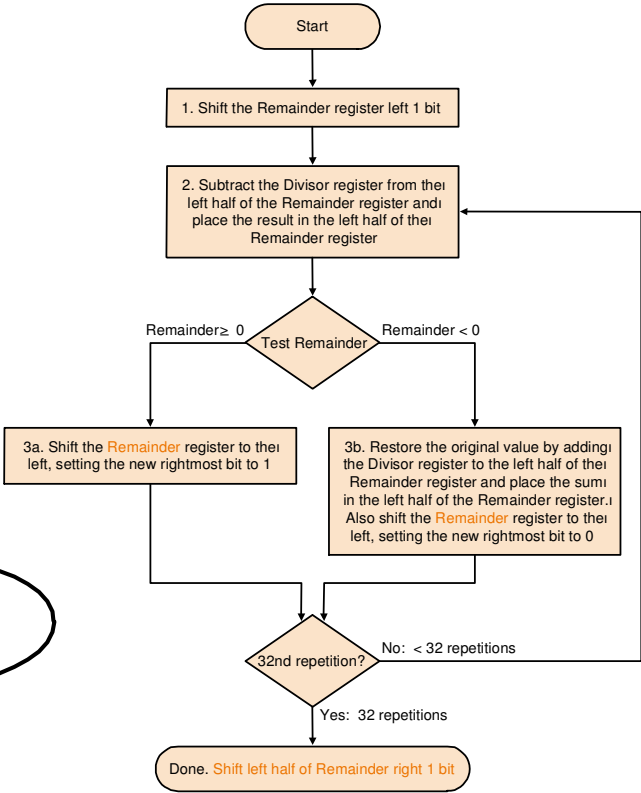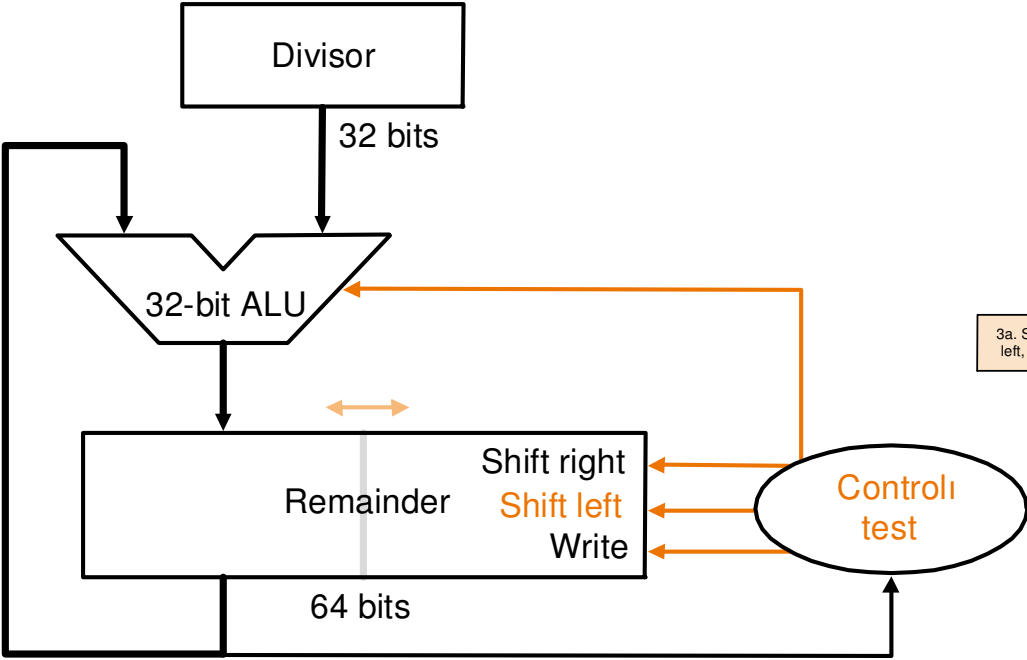Hardware para divisão: terceira alternativa




Instruções

- **No MIPS:**
 - dois novos registradores de uso dedicado para multiplicação: Hi e Lo (32 bits cada)
 - **mult \$t1, \$t2** # Hi Lo \leftarrow \$t1 * \$t2
 - **mfhi \$t1** # \$t1 \leftarrow Hi
 - **mflo \$t1** # \$t1 \leftarrow Lo
- **Para divisão:**
 - **div \$s2, \$s3** # Lo \leftarrow \$s2 / \$s3
 Hi \leftarrow \$s2 mod \$s3
 - **divu \$s2, \$s3** # idem para “unsigned”

Ponto Flutuante

 - **Objetivos:**
 - representação de números não inteiros
 - aumentar a capacidade de representação (maiores ou menores)
- **Formato padronizado**
 $1.XXXXXXXXXX \dots * 2^{yyy}$ (no caso geral B^{yyy})
- **No MIPS:**



sinal-magnitude $(-1)^S F * 2^E$

Ponto Flutuante e padrão IEEE 754

expoente $\in [-128, 127]$

se $2^{10} \approx 10^3$

$$128 = 8 + 10 * 12;$$

$$2^{128} = 2^{(8 + 10 * 12)} = 2^8 * 2^{(10 * 12)} \approx 2 * 10^{38}$$

overflow $\Rightarrow N^\circ > 10^{38}$

underflow $\Rightarrow N^\circ < 10^{-38}$

PADRÃO IEEE 754




mantissa: precisão simples: 23 bits (+1)

precisão dupla: 52 bits (+1)

Padrão IEEE754: bias

$$N^{\circ} = (-1)^S (1 + \text{Mantissa}) * 2^E$$

 Para simplificar a ordenação (sorting): BIAS



No padrão: $2^{(nE - 1)} - 1 = 127$

$$EXP = \text{CAMPO}_{EXP} - \text{BIAS}$$

Exemplo: representar $-0,75_{10} = -(1/2 + 1/4)$

$$-0,75_{10} = -0,11_2 = -1,11 * 2^{-1}$$

mantissa = 1000000 (23 bits)


campo expoente: $-1 + 127 = 126_{10} = 0111\ 1110_2$

1	0111 1110	1000 0000 0000 0000 0000 000
---	-----------	------------------------------


Tabela de faixas de representação do IEEE 754

Precisão simples		Precisão dupla		Significado
Expoente	Mantissa	Expoente	Mantissa	
0	0	0	0	0
0	$\neq 0$	0	$\neq 0$	Número não normalizado
1 – 254	qquer	1 – 2046	qquer	Número normalizado
255	0	2047	0	infinito
255	$\neq 0$	2047	$\neq 0$	NaN (not a number)
8bits	23(+1)	11	52(+1)	


Soma em ponto flutuante

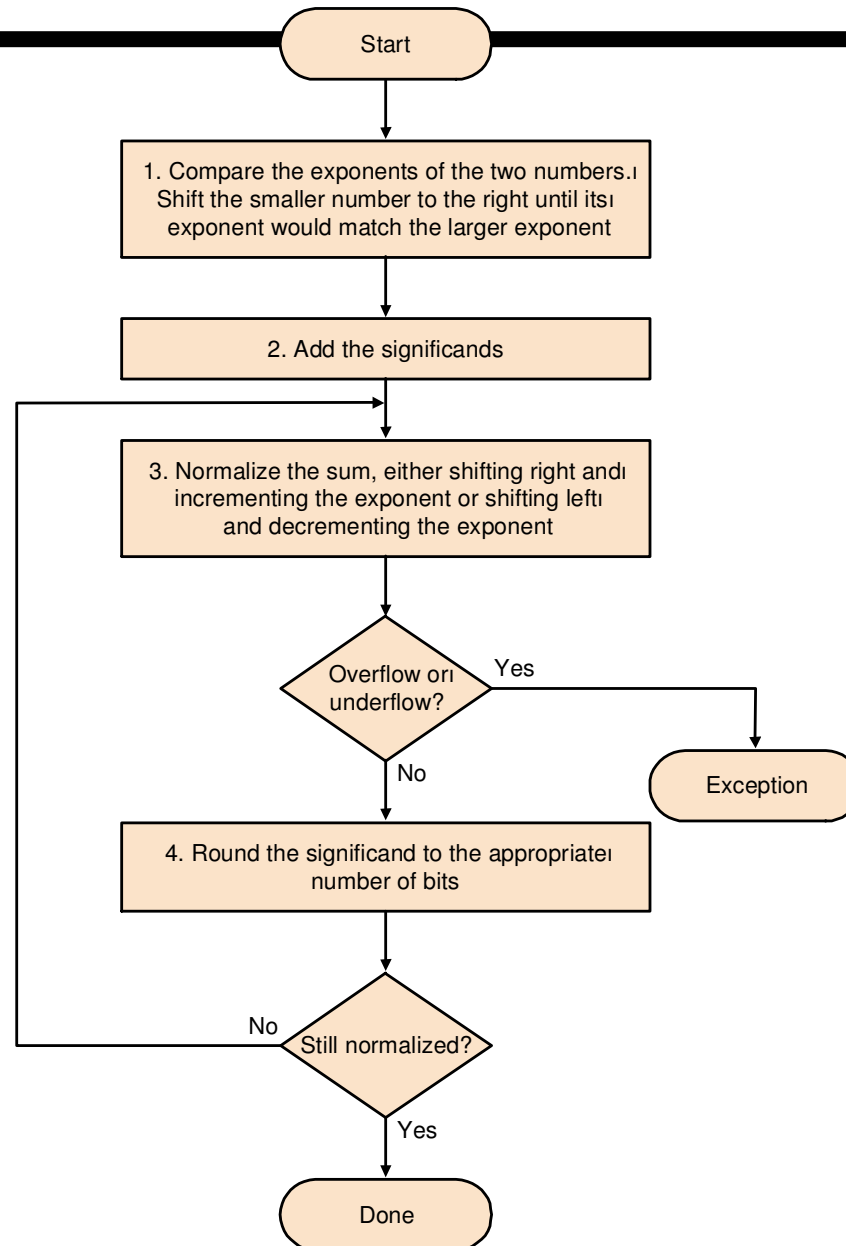

ULA para soma em ponto flutuante

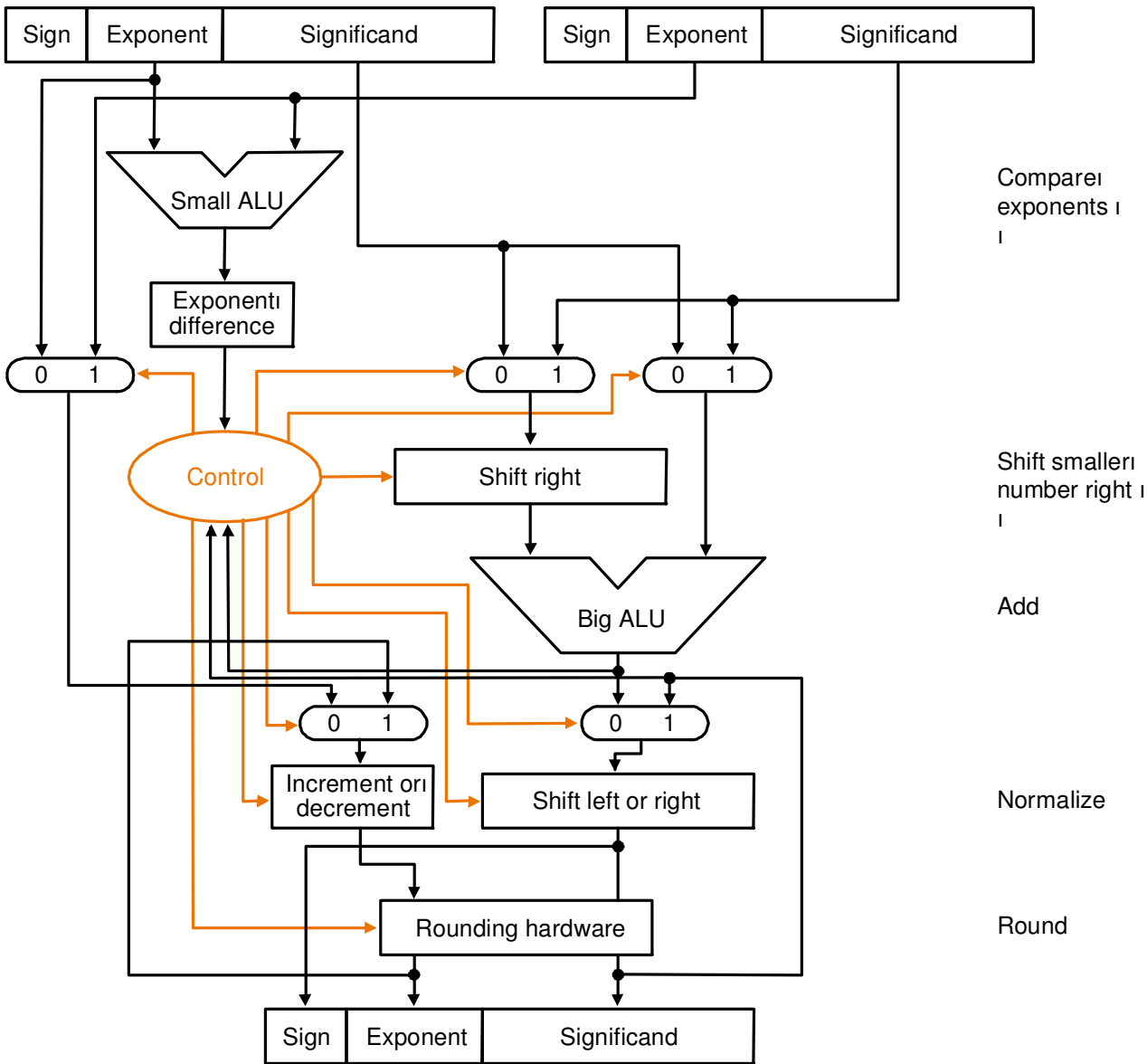

Multiplicação em ponto flutuante

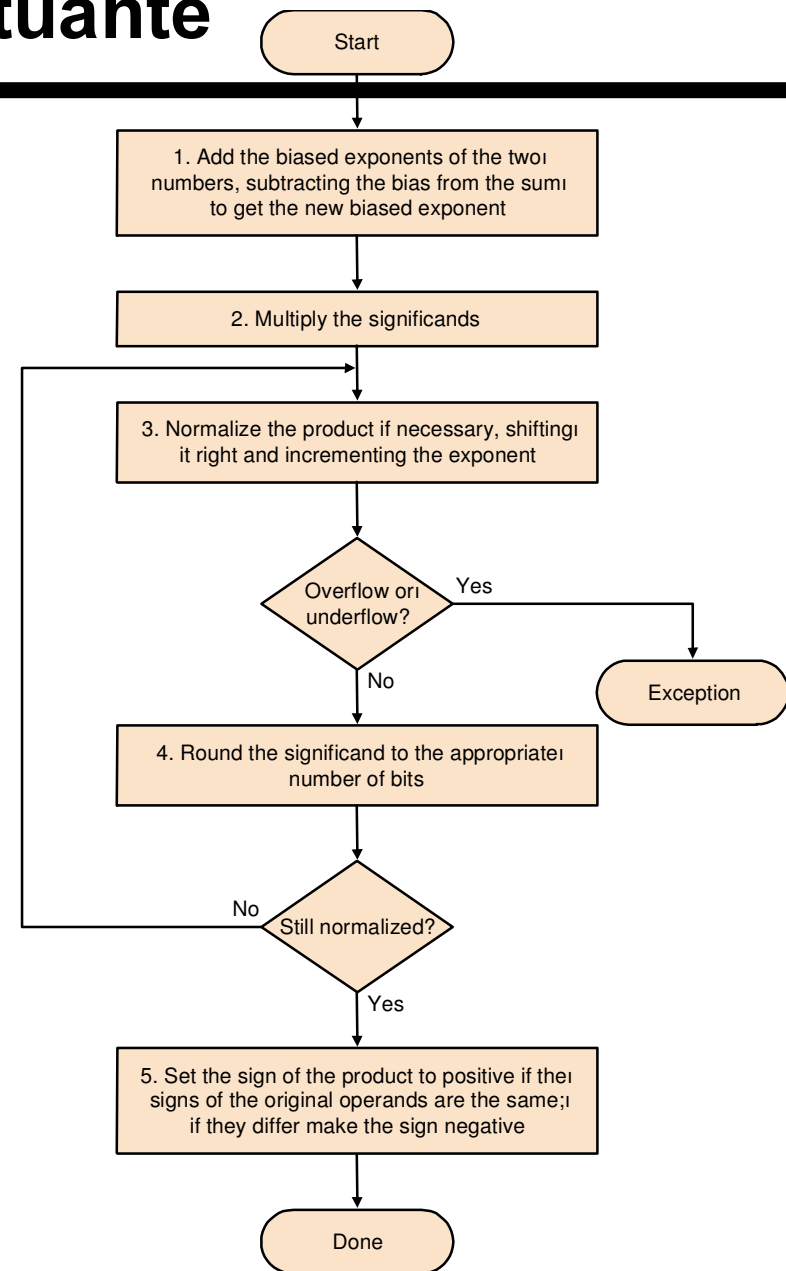

Conjunto de instruções do MIPS para fp

Fig 4.47 Pag 291

Floating Point Complexities

- **Operations are somewhat more complicated (see text)**
- **In addition to overflow we can have “underflow”**
- **Accuracy can be a big problem**
 - **IEEE 754 keeps two extra bits, guard and round**
 - **four rounding modes**
 - **positive divided by zero yields “infinity”**
 - **zero divide by zero yields “not a number”**
 - **other complexities**
- **Implementing the standard can be tricky**
- **Not using the standard can be even worse**
 - **see text for description of 80x86 and Pentium bug!**

Chapter Four Summary

- **Computer arithmetic is constrained by limited precision**
- **Bit patterns have no inherent meaning but standards do exist**
 - **two's complement**
 - **IEEE 754 floating point**
- **Computer instructions determine “meaning” of the bit patterns**
- **Performance and accuracy are important so there are many complexities in real machines (i.e., algorithms and implementation).**

- **We are ready to move on (and implement the processor)**

you may want to look back (Section 4.12 is great reading!)