



MC 602

IC/Unicamp

2011s2

Prof Mario Côrtes

VHDL

Circuitos Aritméticos

Tópicos

- Somador/subtrator
- Somador com overflow
- Diferentes implementações de somadores com VHDL

Full-adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$x_i y_i$ c_i	00	01	11	10
0		1		1
1	1		1	

$$s_{i+1} = x_i \text{ xor } y_i \text{ xor } c_i$$

$x_i y_i$ c_i	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 

Full-adder (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y : IN      STD_LOGIC ;
          s, Cout : OUT     STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
```

Figure 5.23 VHDL code for the full-adder



Full-adder Package (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

PACKAGE fulladd_package IS
  COMPONENT fulladd
    PORT (Cin, x, y      : IN  STD_LOGIC ;
          s, Cout       : OUT   STD_LOGIC ) ;
  END COMPONENT ;
END fulladd_package ;
```


Figure 5.25 Declaration of a package

Somador Ripple Carry

- Atraso para um somador de n bits:

$$t_{\text{ripple}} = Nt_{FA}$$

Onde t_{FA} é o atraso de um full adder

 



4-bit Ripple Carry Adder (sinais)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT ( Cin          : IN     STD_LOGIC ;
          x3, x2, x1, x0 : IN     STD_LOGIC ;
          y3, y2, y1, y0 : IN     STD_LOGIC ;
          s3, s2, s1, s0 : OUT    STD_LOGIC ;
          Cout          : OUT    STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        x => x3, y => y3, Cin => c3, Cout => Cout, s => s3 ) ;
END Structure ;
```

Figure 5.26 Using a package for the four-bit adder



4-bit Ripple Carry Adder (vetores)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout     : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

Figure 5.27 A four-bit adder defined using multibit signals

Descrição Comportamental

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S      : OUT  STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder

Somador/Subtrator

$$K_2 = (\overline{p_{n-1}} \dots \overline{p_0}) + 1 = K_1(P) + 1$$

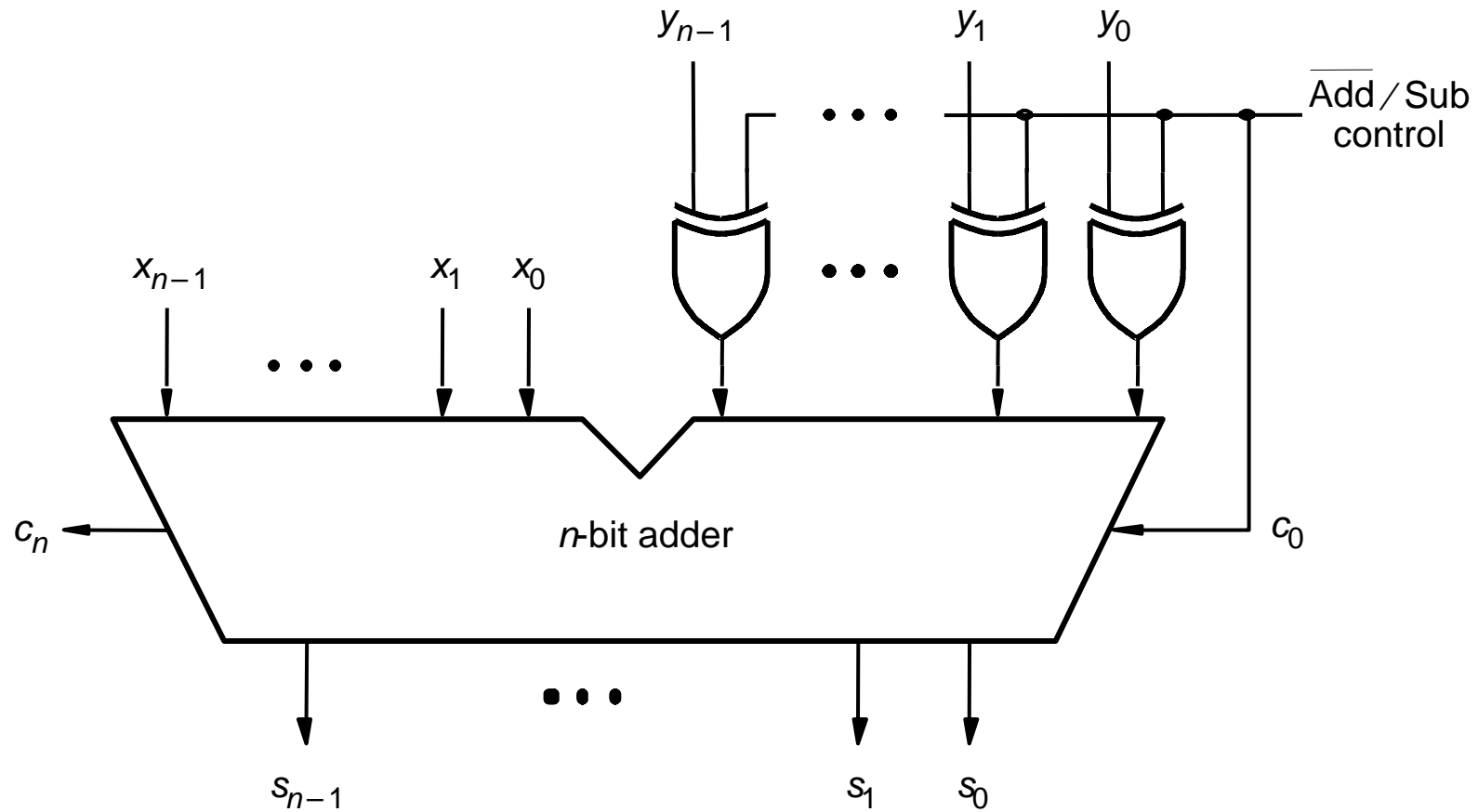


Figure 5.13 Adder/subtractor unit



4-bit Ripple Carry Adder (vetores) + overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout, Overflow : OUT  STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 4) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), C(4) ) ;
    Overflow <= C(3) XOR C(4);
    Cout <= C(4);
END Structure ;
```

Descrição Comportamental

Como incluir overflow?

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          S      : OUT  STD_LOGIC_VECTOR(15 DOWNT0 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder



16-bit Adder com Overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN   STD_LOGIC ;
          X, Y           : IN   STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          S              : OUT  STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          Cout,Overflow  : OUT  STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNT0 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNT0 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```

Figure 5.29 A 16-bit adder with carry and overflow

Codificação em BCD

“No mundo há 10 tipos de pessoas: as que sabem contar em binário e as que não sabem”

BCD

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

Table 5.3 Binary-coded decimal digits

Adição Usando BCD

$$\begin{array}{r}
 X \quad \quad 0111 \quad \quad 7 \\
 + Y \quad + 0101 \quad + 5 \\
 \hline
 Z \quad \quad 1100 \quad 12 \\
 \quad \quad + 0110 \\
 \hline
 \text{carry} \rightarrow 10010 \\
 \quad \quad \underbrace{\quad\quad} \\
 \quad \quad S = 2
 \end{array}$$

$$\begin{array}{r}
 X \quad \quad 1000 \quad \quad 8 \\
 + Y \quad + 1001 \quad + 9 \\
 \hline
 Z \quad \quad 10001 \quad 17 \\
 \quad \quad + 0110 \\
 \hline
 \text{carry} \rightarrow 10111 \\
 \quad \quad \underbrace{\quad\quad} \\
 \quad \quad S = 7
 \end{array}$$

Passou de 10? Remove 10:

$$\begin{aligned}
 S - 10 &= S - 9 - 1 \\
 &= S + K_2(9_{10}) - 1 \\
 &= S + K_1(9_{10}) + 1 - 1 \\
 &= S + \text{not}(1001_2) \\
 &= S + 0110_2 \\
 &= S + 6_{10}
 \end{aligned}$$

Raciocínio Alternativo

Passou de 10?

Remove 10 (carry=1)

$$\begin{aligned}
 S - 10 &= S - (16 - 6) \\
 &= S + 6 - 16 \\
 &= (S + 6) - 16
 \end{aligned}$$

soma

carry

Somador de um Dígito BCD

$$\begin{array}{r}
 z_3 \ z_2 \ z_1 \ z_0 \\
 + 0 \ 1 \ 1 \ 0 \\
 \hline
 \end{array}$$

$C_{out} = 1 ?$

$$C_{out} = d_{out} + z_2 z_3 + z_1 z_3$$

 


Figure 5.40 Circuit for a one-digit BCD adder

Somador em BCD

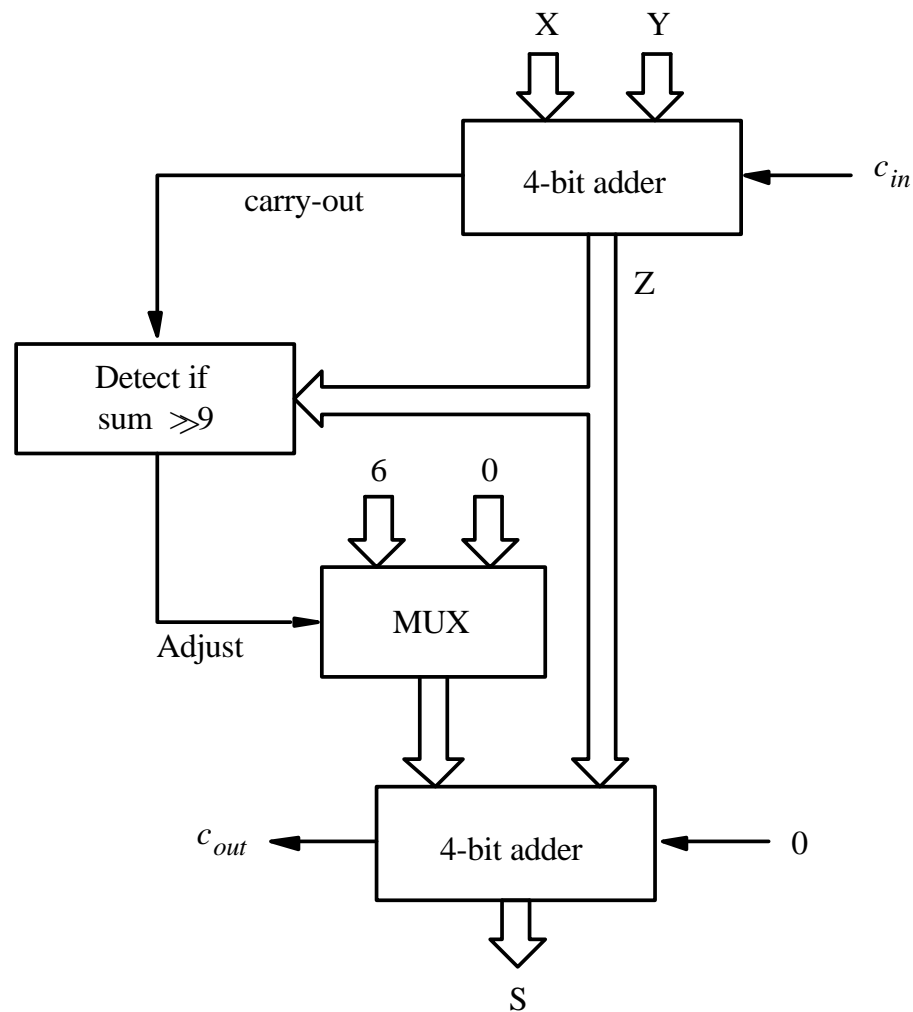


Figure 5.37 Block diagram for a one-digit BCD adder

Somador BCD

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY BCD IS
    PORT ( X, Y: IN STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S: OUT STD_LOGIC_VECTOR(4 DOWNTO 0) ) ;
END BCD ;

ARCHITECTURE Behavior OF BCD IS
    SIGNAL Z : STD_LOGIC_VECTOR(4 DOWNTO 0) ;
    SIGNAL Adjust : STD_LOGIC ;
BEGIN
    Z <= ('0' & X) + Y ;
    Adjust <= '1' WHEN Z > 9 ELSE '0' ;
    S <= Z WHEN (Adjust = '0') ELSE Z + 6 ;
END Behavior ;
```

Figure 5.38 VHDL code for a one-digit BCD adder