



MC 602

IC/Unicamp

2011s2

Prof Mario Côrtes

VHDL

Latches e Flip-Flops



Tópicos

- Uso de processo e memória implícita
- Latches
- FFs
 - Reset síncronos e assíncronos

Descrições em VHDL

- Conceito importante: process

```
PROCESS ( A, B )  
  BEGIN  
    ..... -- corpo do processo  
  END PROCESS
```

- Trecho entre Begin e End é executado sequencialmente (a ordem importa)
- O processo é executado concorrentemente como as demais declarações
- O processo é invocado quando muda algum sinal/variável na lista de sensibilidade



Instanciação de FFD de um pacote

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY altera ;
USE altera.maxplus2.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN      STD_LOGIC ;
          Resetn, Presetn : IN  STD_LOGIC ;
          Q           : OUT   STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Structure OF flipflop IS
BEGIN
    dff_instance: dff PORT MAP
    ( D, Clock, Resetn, Presetn, Q ) ;
END Structure ;
```

Memória implícita

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT ( A, B : IN      STD_LOGIC ;
          AeqB : OUT STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Latch tipo D chaveado

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clk      : IN  STD_LOGIC ;
          Q           : OUT STD_LOGIC) ;
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Flip-Flop tipo D

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT (    D, Clock  : IN  STD_LOGIC ;
           Q          : OUT STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

FFD com Wait Until

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
    PORT ( D, Clock : IN  STD_LOGIC ;
          Q  : OUT  STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        Q <= D ;
    END PROCESS ;
END Behavior ;
```


FFD com Reset assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock      : IN  STD_LOGIC ;
          Q                       : OUT STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

FFD com Reset síncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN STD_LOGIC ;
          Q : OUT STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSE
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```