



IC-UNICAMP

MC 613

IC/Unicamp

Prof Guido Araújo

Prof Mario Côrtes

Circuitos Aritméticos



Tópicos

- Representação sinal-magnitude
- Representação K_1 e K_2
- Somadores half-adder e full-adder
- Somador/subtrator
- Somador com overflow



Representação de Números Negativos

$b_3 \ b_2 \ b_1 \ b_0$	Sinal Magnitude	Complemento de 1	Complemento de 2
0111	+7	7	+7
0110	+6	6	+6
0101	+5	5	+5
0100	+4	4	+4
0011	+3	3	+3
0010	+2	2	+2
0001	+1	1	+1
0000	+0	0	0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Table 5.2 Interpretation of four-bit signed integers



Representação Sinal Magnitude


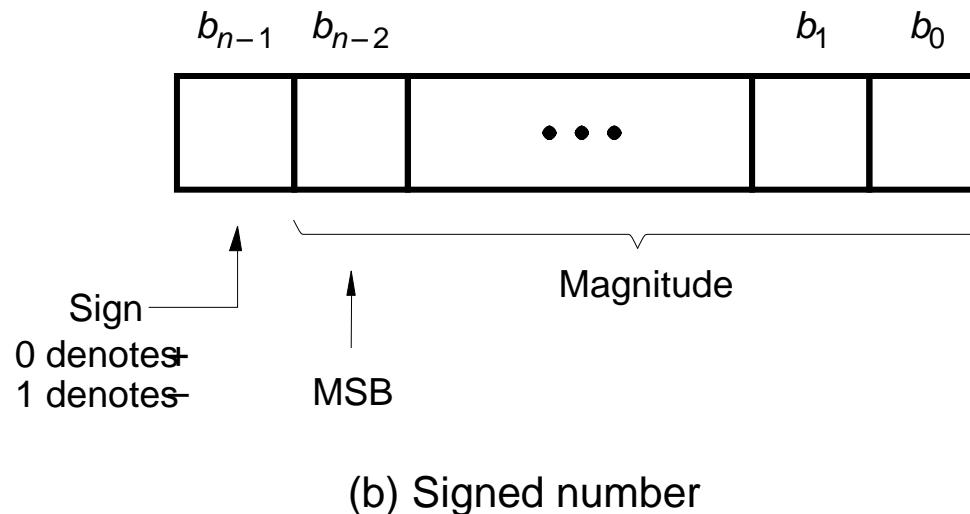


Figure 5.8 Formats for representation of integers

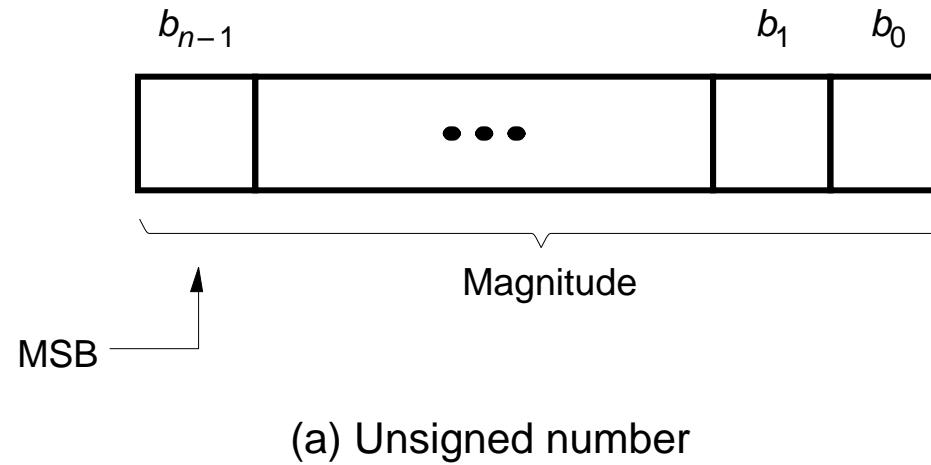

Representação de Números Negativos

- Sinal e Magnitude
 - 1 bit de sinal, $N-1$ bits de magnitude
 - O bit de sinal é o mais significativo (mais a esquerda)
 - Número negativo: 1
 - Número positivo: 0
 - Exemplo, representação de ± 5 com 4-bit:
 - $5 = 1101_2$
 - + $5 = 0101_2$
 - Intervalo de um número N -bit sinal/magnitude:
$$[-(2^{N-1}-1), 2^{N-1}-1]$$



Adição e Subtração Sinal e Magnitude

- Exemplo: $-5 + 5$

$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$

- Duas representações para 0 (± 0):

1000
0000



Representação de Números Negativos

Complemento de 1 (K_1)

Em complemento de “Um” o número negativo K_1 , com n -bits, é obtido subtraíndo seu positivo P de $2^n - 1$

$$K_1 = (2^n - 1) - P$$

Exemplo: se $n = 4$ então:

$$K_1 = (2^4 - 1) - P$$

$$K_1 = (16 - 1) - P$$

$$K_1 = (1111)_2 - P$$

$$P = 7 \rightarrow K_1 = ?$$

$$7 = (0111)_2$$

$$-7 = (1111)_2 - (0111)_2$$

$$-7 = (1000)_2$$



Representação de Números Negativos

- Complemento de 1 (K_1)
 - Regra Prática

$$K_1 = (2^n - 1) - P$$

$$K_1 = 11\dots11 - (p_{n-1} \dots p_0)$$

$$K_1 = (\overline{p}_{n-1} \dots \overline{p}_0)$$



Representação de Números Negativos

Complemento de 2 (K_2)

Em complemento de “Dois” o número negativo K , com n -bits, é obtido subtraíndo seu positivo P de 2^n

$$K_2 = 2^n - P$$

Exemplo: se $n = 4$ então:

$$K_2 = 2^4 - P$$

$$K_2 = 16 - P$$

$$K_2 = (10000)_2 - P$$

$$P = 7 \rightarrow K_2 = ?$$

$$7 = (0111)_2$$

$$-7 = (10000)_2 - (0111)_2$$

$$-7 = (1001)_2$$



Representação de Números Negativos

- Complemento de 2 (K_2)
 - Regra Prática

$$K_2 = 2^n - P \quad \longrightarrow \quad K_2 = (2^n - 1) + 1 - P$$

$$K_2 = (2^n - 1) - P + 1$$

$$K_2 = 11\dots11 - (p_{n-1} \dots p_0) + 1$$

$$K_2 = (\overline{p}_{n-1} \dots \overline{p}_0) + 1 = K_1(P) + 1$$



Representação de Números Negativos

- Complemento de 2 (K_2)
 - Maior número positivo de 4-bit: 0111_2 (7_{10})
 - Maior número negativo de 4-bit: 1000_2 ($-2^3 = -8_{10}$)
 - O most significant bit também indica o sinal (1 = negativo, 0 = positivo)
 - Intervalo de um número de N -bit: $[-2^{N-1}, 2^{N-1}-1]$



Adição em K₂

$$\begin{array}{r} (+5) \\ + (+2) \\ \hline (+7) \end{array}$$

$$\begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array}$$

$$\begin{array}{r} (-5) \\ + (+2) \\ \hline (-3) \end{array}$$

$$\begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$$

$$\begin{array}{r} (+5) \\ + (-2) \\ \hline (+3) \end{array}$$

$$\begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \end{array}$$

$$\begin{array}{r} (-5) \\ + (-2) \\ \hline (-7) \end{array}$$

$$\begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \end{array}$$

ignore

ignore

Figure 5.10 Examples of 2's complement addition



Subtração em K₂

$$\begin{array}{r} (+5) \\ - (-2) \\ \hline (+7) \end{array} \quad \begin{array}{r} 0101 \\ - 1110 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array} \quad \begin{array}{r} (+5) \\ - (+2) \\ \hline (+3) \end{array} \quad \begin{array}{r} 0101 \\ - 0010 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \end{array}$$

↑
ignore

$$\begin{array}{r} (-5) \\ - (-2) \\ \hline (-3) \end{array} \quad \begin{array}{r} 1011 \\ - 1110 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array} \quad \begin{array}{r} (-5) \\ - (+2) \\ \hline (-7) \end{array} \quad \begin{array}{r} 1011 \\ - 0010 \\ \hline \end{array} \quad \Rightarrow \quad \begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \end{array}$$

↑
ignore

Figure 5.11 Examples of 2's complement subtraction



Half-adder


$$\begin{array}{r} x \\ +y \\ \hline c\ s \end{array}$$

↑ ↑
Carry Sum


(a) The four possible cases

x	y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

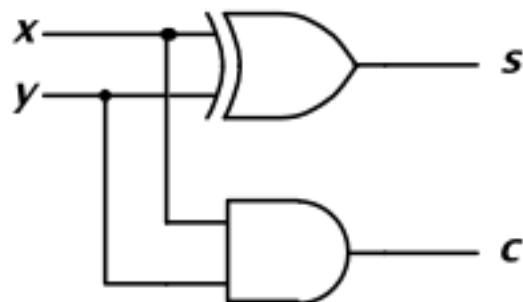


(c) Circuit

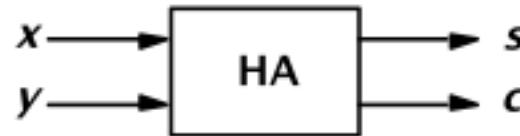


(d) Graphical symbol



Somador com Half-adder

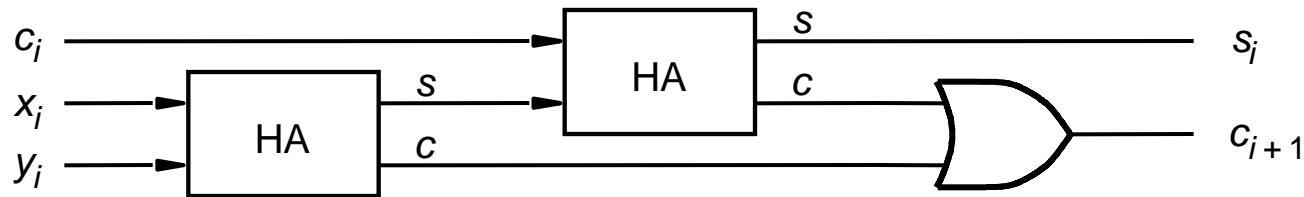

(a) Block diagram

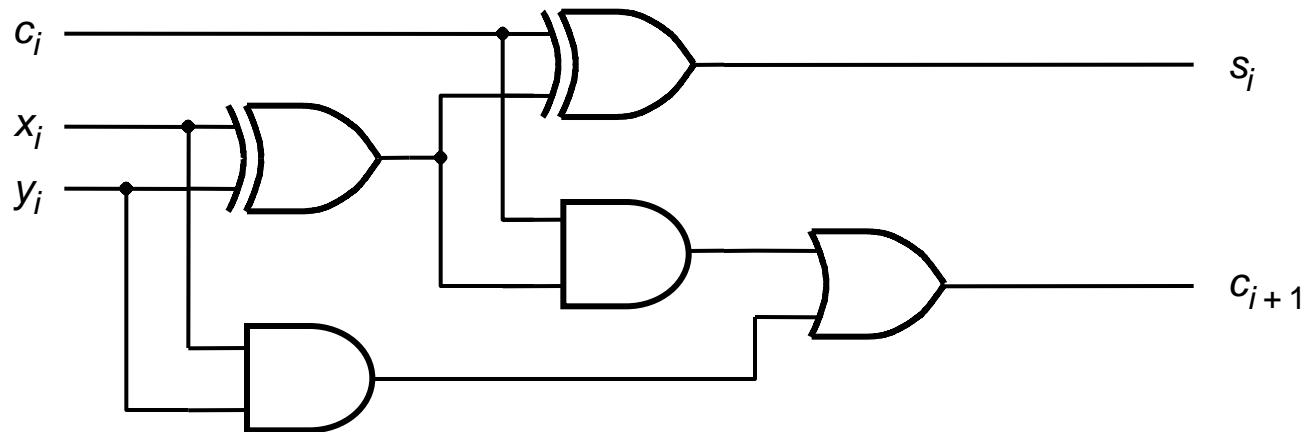


(b) Detailed diagram

Figure 5.5 A decomposed implementation of the full-adder circuit



Full-adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

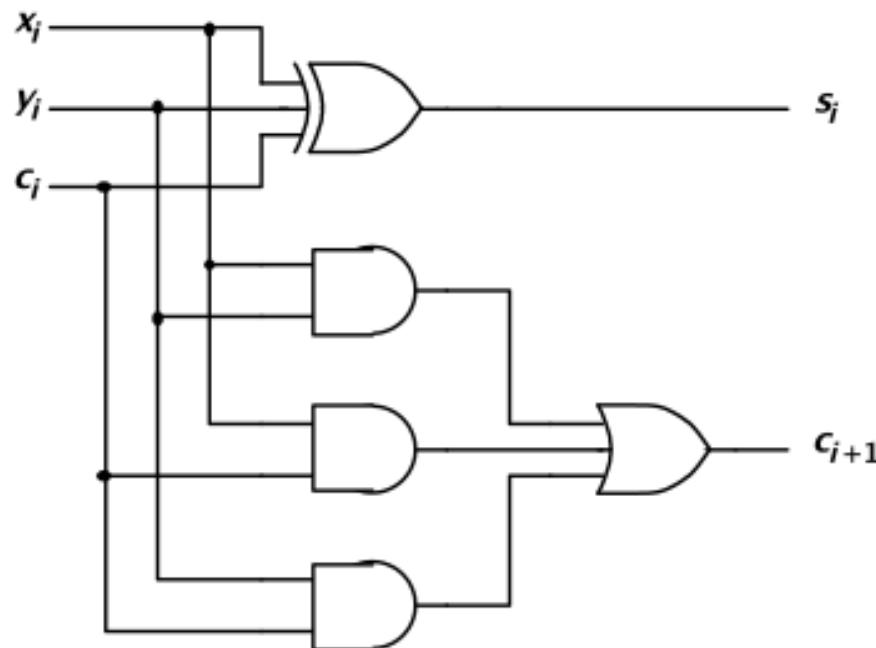

$x_i \cdot y_i$	00	01	11	10
c_i	0			
0		1		1
1	1		1	

$$s_{i+1} = x_i \oplus y_i \oplus c_i$$

$x_i \cdot y_i$	00	01	11	10
c_i	0			
0			1	
1		1	1	1

$$c_{i+1} = x_i \cdot y_i + x_i \cdot c_i + y_i \cdot c_i$$

(b) Karnaugh maps



Full-adder (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT (          Cin, x, y      : IN
                  s, Cout   : OUT      STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
```

Figure 5.23 VHDL code for the full-adder



Full-adder Package (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

PACKAGE fulladd_package IS
    COMPONENT fulladd
        PORT (Cin, x, y      : IN  STD_LOGIC ;
              s, Cout       : OUT     STD_LOGIC ) ;
    END COMPONENT ;
END fulladd_package ;
```

Figure 5.25 Declaration of a package




Somador Ripple Carry

- Atraso para um somador de n bits:

$$t_{\text{ripple}} = N t_{FA}$$

Onde t_{FA} é o atraso de um full adder

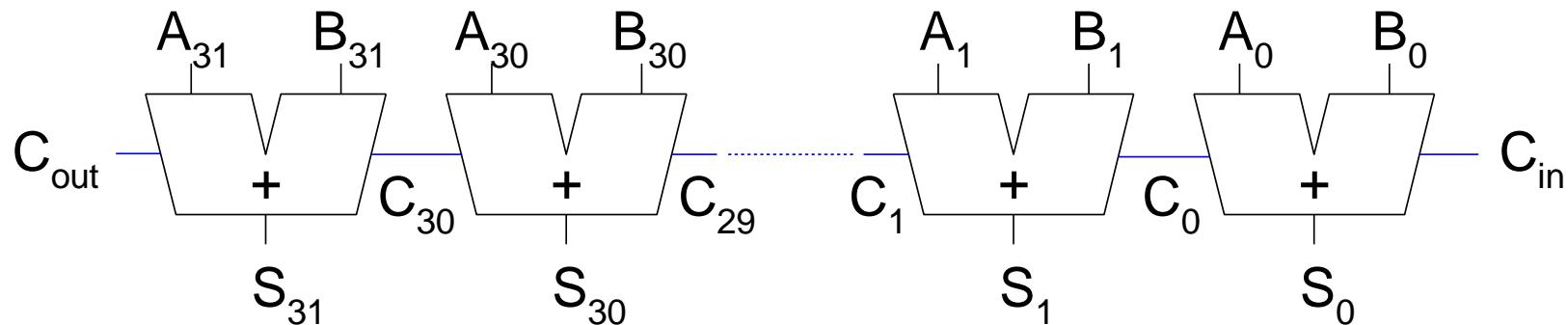



4-bit Ripple Carry Adder (sinais)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT ( Cin           : IN      STD_LOGIC ;
           x3, x2, x1, x0   : IN      STD_LOGIC ;
           y3, y2, y1, y0   : IN      STD_LOGIC ;
           s3, s2, s1, s0   : OUT     STD_LOGIC ;
           Cout            : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        x => x3, y => y3, Cin => c3, Cout => Cout, s => s3 ) ;
END Structure ;
```

Figure 5.26 Using a package for the four-bit adder



4-bit Ripple Carry Adder (vetores)

IC-UNICAMP

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout    : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

Figure 5.27 A four-bit adder defined using multibit signals



Descrição Comportamental

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           S      : OUT STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder



Somador/Subtrator

$$K_2 = (\overline{p_{n-1}} \dots \overline{p_0}) + 1 = K_1(P) + 1$$

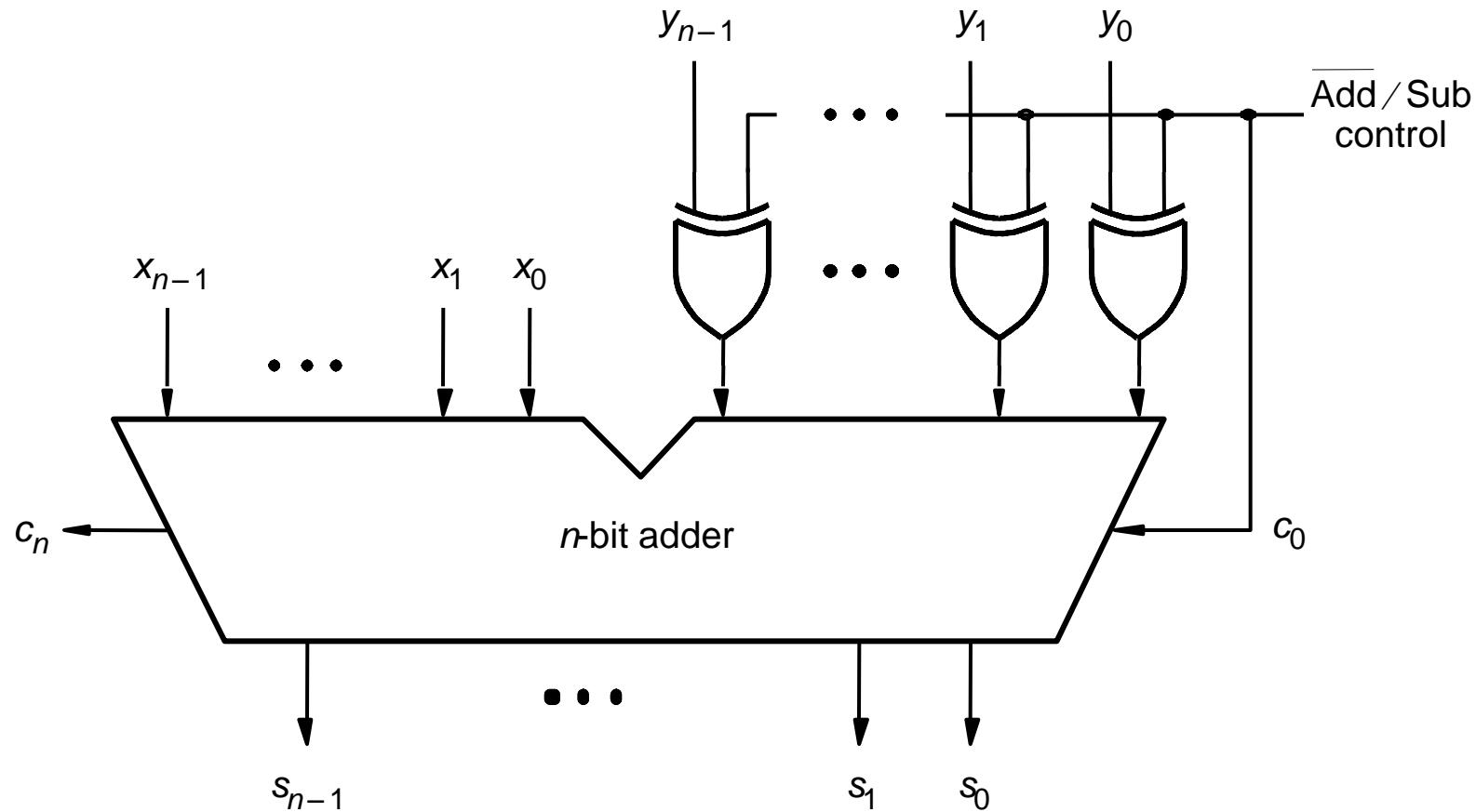


Figure 5.13 Adder/subtractor unit




Overflow (Soma)

- $A + B$
 - $\text{sign}(A) = \text{sign}(B)$: overflow **possível**
 - $\text{sign}(A) \neq \text{sign}(B)$: overflow impossível

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array} \quad \begin{array}{r} 0111 \\ + 0010 \\ \hline 1001 \end{array}$$
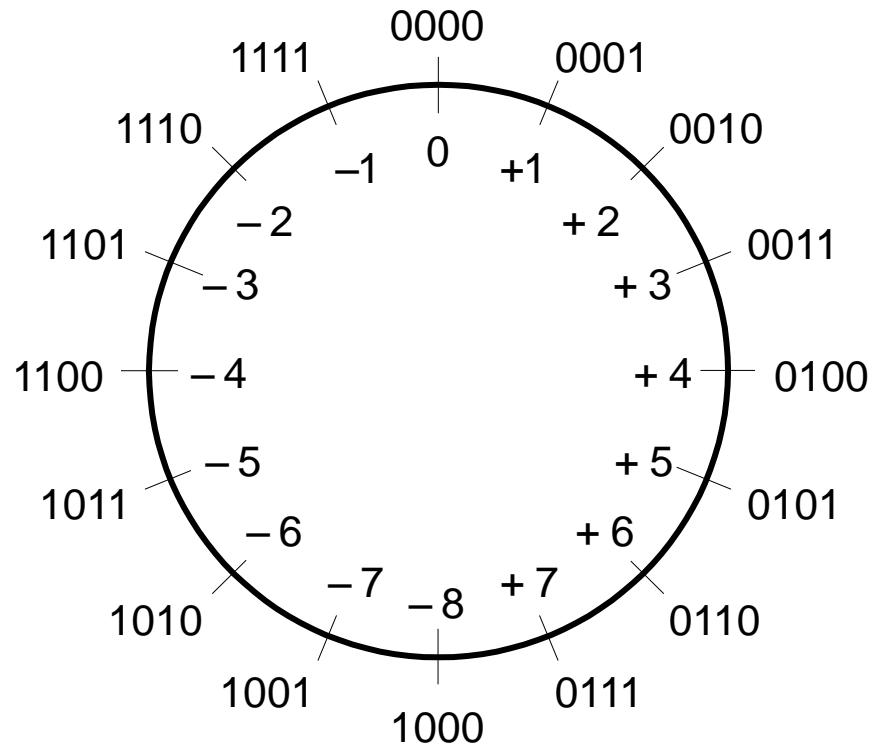
$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array} \quad \begin{array}{r} 1001 \\ + 0010 \\ \hline 1011 \end{array}$$






Overflow (Subtração)

- $A - B = A + (-B)$, reduz à soma
 - $\text{sign}(A) = \text{sign}(B)$: overflow impossível
 - $\text{sign}(A) \neq \text{sign}(B)$: overflow **possível**

$$\begin{array}{r} (+7) \\ - (+2) \\ \hline (+5) \end{array} \quad \begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array} \quad \begin{array}{r} 0111 \\ + 1110 \\ \hline 10101 \end{array}$$
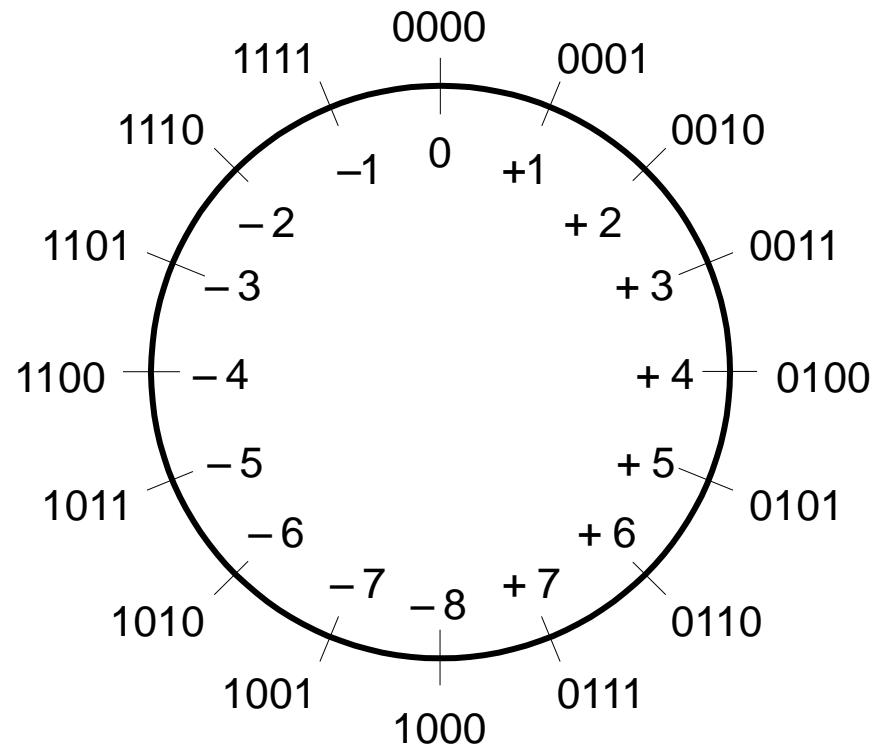
$$\begin{array}{r} (-7) \\ - (+2) \\ \hline (-5) \end{array} \quad \begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array} \quad \begin{array}{r} 1001 \\ + 1110 \\ \hline 10111 \end{array}$$





Resumo Overflow

A	B	$S = A + B$	OV
+	-	+	0
+	-	-	0
-	+	+	0
-	+	-	0
+	+	+	0
+ (highlighted)	+	-	1
- (highlighted)	-	+	1
-	-	-	0

$$\begin{array}{r}
 1 \\
 0 x.. \\
 + 1 x.. \\
 \hline
 1 0 x..
 \end{array}$$

$$\begin{array}{r}
 1 \\
 0 x.. \\
 + 0 x.. \\
 \hline
 0 1 x..
 \end{array}$$

$$\begin{array}{r}
 0 \\
 1 x.. \\
 + 1 x.. \\
 \hline
 1 0 x..
 \end{array}$$

$$\begin{array}{r}
 0 \\
 0 x.. \\
 + 1 x.. \\
 \hline
 0 1 x..
 \end{array}$$

$$\begin{array}{r}
 0 \\
 0 x.. \\
 + 0 x.. \\
 \hline
 0 0 x..
 \end{array}$$

$$\begin{array}{r}
 1 \\
 1 x.. \\
 + 1 x.. \\
 \hline
 1 1 x..
 \end{array}$$

$$V = C_n(S) \text{ xor } C_{n-1}(S)$$



Overflow em K₂

$$\begin{array}{r} (+7) \\ + (+2) \\ \hline (+9) \end{array}$$

$$\begin{array}{r} 0111 \\ + 0010 \\ \hline 1001 \end{array}$$

$$\begin{array}{r} (-7) \\ + (+2) \\ \hline (-5) \end{array}$$

$$\begin{array}{r} 1001 \\ + 0010 \\ \hline 1011 \end{array}$$

$$\begin{array}{l} c_4 = 0 \\ c_3 = 1 \end{array}$$

$$\begin{array}{l} c_4 = 0 \\ c_3 = 0 \end{array}$$

$$\begin{array}{r} (+7) \\ + (-2) \\ \hline (+5) \end{array}$$

$$\begin{array}{r} 0111 \\ + 1110 \\ \hline 10101 \end{array}$$

$$\begin{array}{r} (-7) \\ + (-2) \\ \hline (-9) \end{array}$$

$$\begin{array}{r} 1001 \\ + 1110 \\ \hline 10111 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 1 \end{array}$$

$$\begin{array}{l} c_4 = 1 \\ c_3 = 0 \end{array}$$

Figure 5.14 Examples of determination of overflow



4-bit Ripple Carry Adder (vetores) + overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout, Overflow : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 4) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), C(4) ) ;
    Overflow <= C(3) XOR C(4) ;
    Cout <= C(4) ;
END Structure ;
```



Descrição Comportamental

Como incluir overflow?

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           S      : OUT STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder



16-bit Adder com Overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN STD_LOGIC ;
           X, Y         : IN STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           S            : OUT STD_LOGIC_VECTOR(15 DOWNTO 0) ;
           Cout,Overflow : OUT STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNTO 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNTO 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```

Figure 5.29 A 16-bit adder with carry and overflow



Somador Ripple Carry

- Atraso para um somador de n bits:

$$t_{\text{ripple}} = N t_{FA}$$

Onde t_{FA} é o atraso de um full adder

