



MC 613

IC/Unicamp

Prof Guido Araújo

Prof Mario Côrtes

Circuitos Aritméticos

Tópicos


- Representação sinal-magnitude
- Representação K_1 e K_2
- Somadores half-adder e full-adder
- Somador/subtrator
- Somador com overflow

Representação de Números Negativos


b₃ b₂ b₁ b₀	Sinal Magnitude	Complemento de 1	Complemento de 2
0111	+7	7	+7
0110	+6	6	+6
0101	+5	5	+5
0100	+4	4	+4
0011	+3	3	+3
0010	+2	2	+2
0001	+1	1	+1
0000	+0	0	0
1000	-0	-7	-8
1001	-1	-6	-7
1010	-2	-5	-6
1011	-3	-4	-5
1100	-4	-3	-4
1101	-5	-2	-3
1110	-6	-1	-2
1111	-7	-0	-1

Table 5.2 Interpretation of four-bit signed integers

Representação Sinal Magnitude

 

(a) Unsigned number

 

(b) Signed number

Figure 5.8 Formats for representation of integers

Representação de Números Negativos

- Sinal e Magnitude
 - 1 bit de sinal, $N-1$ bits de magnitude
 - O bit de sinal é o mais significativo (mais a esquerda)
 - Número negativo: 1
 - Número positivo: 0
 - Exemplo, representação de ± 5 com 4-bit:
 - $-5 = 1101_2$
 - $+5 = 0101_2$
 - Intervalo de um número N -bit sinal/magnitude:
 - $[-(2^{N-1}-1), 2^{N-1}-1]$



Adição e Subtração Sinal e Magnitude

- Exemplo: $-5 + 5$

$$\begin{array}{r} 1101 \\ + 0101 \\ \hline 10010 \end{array}$$

- Duas representações para 0 (± 0):

$$\begin{array}{r} 1000 \\ 0000 \end{array}$$



Representação de Números Negativos

Complemento de 1 (K_1)

Em complemento de “Um” o número negativo K_1 , com n -bits, é obtido subtraindo seu positivo P de $2^n - 1$

$$K_1 = (2^n - 1) - P$$

Exemplo: se $n = 4$ então:

$$K_1 = (2^4 - 1) - P$$

$$K_1 = (16 - 1) - P$$

$$K_1 = (1111)_2 - P$$

$$P = 7 \rightarrow K_1 = ?$$

$$7 = (0111)_2$$

$$-7 = (1111)_2 - (0111)_2$$

$$-7 = (1000)_2$$

Representação de Números Negativos

- Complemento de 1 (K_1)
 - Regra Prática

$$K_1 = (2^n - 1) - P$$

$$K_1 = 11\dots 11 - (p_{n-1} \dots p_0)$$

$$K_1 = \overline{p_{n-1}} \dots \overline{p_0}$$

Representação de Números Negativos

Complemento de 2 (K_2)

Em complemento de “Dois” o número negativo K , com n -bits, é obtido subtraindo seu positivo P de 2^n

$$K_2 = 2^n - P$$

Exemplo: se $n = 4$ então:

$$K_2 = 2^4 - P$$

$$K_2 = 16 - P$$

$$K_2 = (10000)_2 - P$$

$$P = 7 \rightarrow K_2 = ?$$

$$7 = (0111)_2$$

$$-7 = (10000)_2 - (0111)_2$$

$$-7 = (1001)_2$$

Representação de Números Negativos

- Complemento de 2 (K_2)
 - Regra Prática

$$K_2 = 2^n - P \quad \longrightarrow \quad K_2 = (2^n - 1) + 1 - P$$
$$K_2 = (2^n - 1) - P + 1$$

$$K_2 = 11 \dots 11 - (p_{n-1} \dots p_0) + 1$$

$$K_2 = \overline{(p_{n-1} \dots p_0)} + 1 = K_1(P) + 1$$



Representação de Números Negativos

- Complemento de 2 (K_2)
 - Maior número positivo de 4-bit: 0111_2 (7_{10})
 - Maior número negativo de 4-bit: 1000_2 ($-2^3 = -8_{10}$)
 - O most significant bit também indica o sinal (1 = negativo, 0 = positivo)
 - Intervalo de um número de N -bit: $[-2^{N-1}, 2^{N-1}-1]$

Adição em K_2

(+ 5)	0 1 0 1	(-5)	1 0 1 1
+ (+ 2)	+ 0 0 1 0	+ (+ 2)	+ 0 0 1 0
<hr style="border: 0.5px solid black;"/>			
(+ 7)	0 1 1 1	(-3)	1 1 0 1

(+ 5)	0 1 0 1	(-5)	1 0 1 1
+ (-2)	+ 1 1 1 0	+ (-2)	+ 1 1 1 0
<hr style="border: 0.5px solid black;"/>			
(+ 3)	1 0 0 1 1	(-7)	1 1 0 0 1
	↑		↑
	ignore		ignore

Figure 5.10 Examples of 2's complement addition

Subtração em K_2

$\begin{array}{r} (+5) \quad 0101 \\ - (-2) \quad -1110 \\ \hline (+7) \end{array}$	\Rightarrow	$\begin{array}{r} 0101 \\ + 0010 \\ \hline 0111 \end{array}$	$\begin{array}{r} (+5) \quad 0101 \\ - (+2) \quad -0010 \\ \hline (+3) \end{array}$	\Rightarrow	$\begin{array}{r} 0101 \\ + 1110 \\ \hline 10011 \\ \uparrow \\ \text{ignore} \end{array}$
$\begin{array}{r} (-5) \quad 1011 \\ - (-2) \quad -1110 \\ \hline (-3) \end{array}$	\Rightarrow	$\begin{array}{r} 1011 \\ + 0010 \\ \hline 1101 \end{array}$	$\begin{array}{r} (-5) \quad 1011 \\ - (+2) \quad -0010 \\ \hline (-7) \end{array}$	\Rightarrow	$\begin{array}{r} 1011 \\ + 1110 \\ \hline 11001 \\ \uparrow \\ \text{ignore} \end{array}$

Figure 5.11 Examples of 2's complement subtraction

Half-adder


x	0	0	1	1
$+y$	$+0$	$+1$	$+0$	$+1$
$c\ s$	00	01	01	10

Carry
↑
↑
Sum


(a) The four possible cases

x	y	Carry c	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 


(c) Circuit

 


(d) Graphical symbol

Somador com Half-adder

 

(a) Block diagram

 

(b) Detailed diagram

Figure 5.5 A decomposed implementation of the full-adder circuit

Full-adder

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1


$c_i \backslash x_i y_i$	00	01	11	10
0		1		1
1	1		1	

$$s_{i+1} = x_i \text{ XOR } y_i \text{ XOR } c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

(b) Karnaugh maps

 



Full-adder (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y : IN      STD_LOGIC ;
          s, Cout : OUT     STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
```

Figure 5.23 VHDL code for the full-adder

Full-adder Package (VHDL)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

PACKAGE fulladd_package IS
  COMPONENT fulladd
    PORT (Cin, x, y      : IN  STD_LOGIC ;
          s, Cout       : OUT   STD_LOGIC ) ;
  END COMPONENT ;
END fulladd_package ;
```


Figure 5.25 Declaration of a package

Somador Ripple Carry

- Atraso para um somador de n bits:

$$t_{\text{ripple}} = Nt_{FA}$$

Onde t_{FA} é o atraso de um full adder

 



4-bit Ripple Carry Adder (sinais)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT ( Cin          : IN     STD_LOGIC ;
           x3, x2, x1, x0 : IN     STD_LOGIC ;
           y3, y2, y1, y0 : IN     STD_LOGIC ;
           s3, s2, s1, s0 : OUT    STD_LOGIC ;
           Cout          : OUT    STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        x => x3, y => y3, Cin => c3, Cout => Cout, s => s3 ) ;
END Structure ;
```

Figure 5.26 Using a package for the four-bit adder



4-bit Ripple Carry Adder (vetores)

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout     : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

Figure 5.27 A four-bit adder defined using multibit signals



Descrição Comportamental

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S      : OUT  STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder

Somador/Subtrator

$$K_2 = (\overline{p_{n-1}} \dots \overline{p_0}) + 1 = K_1(P) + 1$$

 



Figure 5.13 Adder/subtractor unit

Overflow (Soma)

- $A + B$
 - $\text{sign}(A) = \text{sign}(B)$: overflow **possível**
 - $\text{sign}(A) \neq \text{sign}(B)$: overflow impossível

$$\begin{array}{r}
 (+7) \quad 0111 \\
 + (+2) \quad +0010 \\
 \hline
 (+9) \quad 1001
 \end{array}$$
 
$$\begin{array}{r}
 (-7) \quad 1001 \\
 + (+2) \quad +0010 \\
 \hline
 (-5) \quad 1011
 \end{array}$$




Overflow (Subtração)

- $A - B = A + (-B)$, reduz à soma
 - $\text{sign}(A) = \text{sign}(B)$: overflow impossível
 - $\text{sign}(A) \neq \text{sign}(B)$: overflow **possível**

$(+7)$	$(+7)$	0111
$- (+2)$	$+ (-2)$	$+ 1110$
$(+5)$	$(+5)$	10101

(-7)	(-7)	1001
$- (+2)$	$+ (-2)$	$+ 1110$
(-5)	(-9)	10111

 

Resumo Overflow

A	B	S = A + B	OV
+	-	+	0
+	-	-	0
-	+	+	0
-	+	-	0
+	+	+	0
+	+	-	1
-	-	+	1
-	-	-	0

$$\begin{array}{r} 1 \\ 0 \text{ x..} \\ + 1 \text{ x..} \\ \hline 1 \ 0 \text{ x..} \end{array}$$

$$\begin{array}{r} 0 \\ 0 \text{ x..} \\ + 1 \text{ x..} \\ \hline 0 \ 1 \text{ x..} \end{array}$$

$$\begin{array}{r} 1 \\ 0 \text{ x..} \\ + 0 \text{ x..} \\ \hline 0 \ 1 \text{ x..} \end{array}$$

$$\begin{array}{r} 0 \\ 0 \text{ x..} \\ + 0 \text{ x..} \\ \hline 0 \ 0 \text{ x..} \end{array}$$

$$\begin{array}{r} 0 \\ 1 \text{ x..} \\ + 1 \text{ x..} \\ \hline 1 \ 0 \text{ x..} \end{array}$$

$$\begin{array}{r} 1 \\ 1 \text{ x..} \\ + 1 \text{ x..} \\ \hline 1 \ 1 \text{ x..} \end{array}$$

$$V = C_n(S) \text{ xor } C_{n-1}(S)$$

Overflow em K_2

(+ 7)	0 1 1 1	(-7)	1 0 0 1
<u>+ (+ 2)</u>	<u>+ 0 0 1 0</u>	<u>+ (+ 2)</u>	<u>+ 0 0 1 0</u>
(+ 9)	1 0 0 1	(-5)	1 0 1 1
	$c_4 = 0$		$c_4 = 0$
	$c_3 = 1$		$c_3 = 0$
(+ 7)	0 1 1 1	(-7)	1 0 0 1
<u>+ (-2)</u>	<u>+ 1 1 1 0</u>	<u>+ (-2)</u>	<u>+ 1 1 1 0</u>
(+ 5)	1 0 1 0 1	(-9)	1 0 1 1 1
	$c_4 = 1$		$c_4 = 1$
	$c_3 = 1$		$c_3 = 0$

Figure 5.14 Examples of determination of overflow



4-bit Ripple Carry Adder (vetores) + overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT (Cin      : IN      STD_LOGIC ;
          X, Y     : IN      STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S        : OUT     STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout, Overflow : OUT   STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 4) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), C(4) ) ;
    Overflow <= C(3) XOR C(4);
    Cout <= C(4);
END Structure ;
```

Descrição Comportamental

Como incluir overflow?

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S      : OUT  STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

Figure 5.28 VHDL code for a 16-bit adder



16-bit Adder com Overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( Cin          : IN    STD_LOGIC ;
          X, Y          : IN    STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          S             : OUT   STD_LOGIC_VECTOR(15 DOWNT0 0) ;
          Cout,Overflow : OUT   STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNT0 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNT0 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```

Figure 5.29 A 16-bit adder with carry and overflow

Somador Ripple Carry

- Atraso para um somador de n bits:

$$t_{\text{ripple}} = Nt_{FA}$$

Onde t_{FA} é o atraso de um full adder

