


Chapter Five

The Processor: Datapath & Control

- We're ready to look at an implementation of the MIPS
 - Simplified to contain only:
 - memory-reference instructions: lw, sw
 - arithmetic-logical instructions: add, sub, and, or, slt
 - control flow instructions: beq, j
 - Generic Implementation:
 - use the program counter (PC) to supply instruction address
 - get the instruction from memory
 - read registers
 - use the instruction to decide exactly what to do
 - All instructions use the ALU after reading the registers
 - Why? memory-reference? arithmetic? control flow?
- Handwritten notes:* beq \$t1, \$t2, LABEL; Enderego; Operand

More Implementation Details

Abstract / Simplified View:

 


Two types of functional units:

- elements that operate on data values (combinational)
- elements that contain state (sequential)

State Elements

 - Unlocked vs. Clocked
- Clocks used in synchronous logic
 - when should an element that contains state be updated?




Our Implementation

An edge triggered methodology


Typical execution:

 - read contents of some state elements,
- send values through some combinational logic
- write results to one or more state elements




Register File

Built using D flip-flops

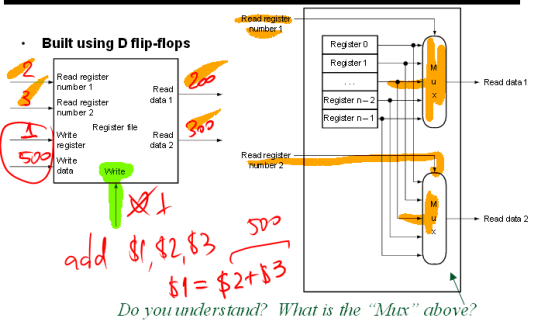

Abstraction

 
- Make sure you understand the abstractions!
- Sometimes it is easy to think you do, when you don't



11

Register File

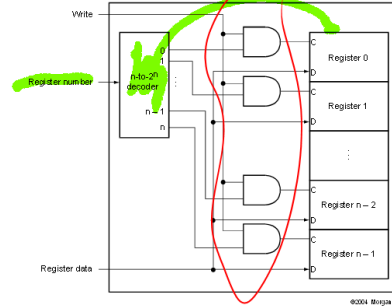
- Note: we still use the real clock to determine when to write



12

Simple Implementation

 
- Include the functional units we need for each instruction



13

Simple Implementation

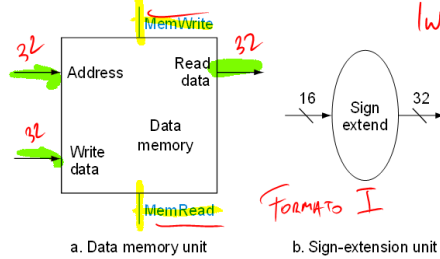
- Include the functional units we need for each instruction



14

Simple Implementation

 
- Include the functional units we need for each instruction



15

Building the Datapath

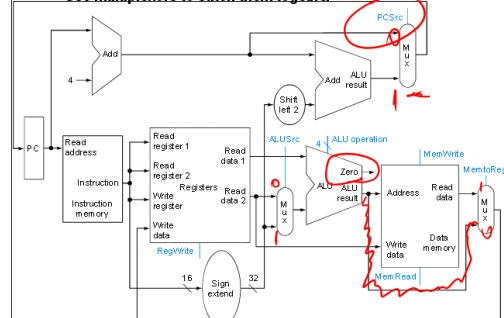
- Use multiplexers to stitch them together



16

Control

 
- Selecting the operations to perform (ALU, read/write, etc.)
- Controlling the flow of data (multiplexor inputs)
- Information comes from the 32 bits of the instruction
- Example:



- ALU's operation based on instruction type and function code

Control

 - e.g., what should the ALU do with this instruction
- Example: lw \$1, 100(\$2)



- ALU control input

0000	AND
0001	OR
0010	add
0110	subtract
0111	set-on-less-than
1100	NOR

- Why is the code for subtract 0110 and not 0011?



Control

- Must describe hardware to compute 4-bit ALU control input
 - given instruction type
 - 00 = lw, sw
 - 01 = beq
 - 10 = arithmetic
- Describe it using a truth table (can turn into gates):

ALUOp		Function field						Operation
ALUOp0	ALUOp1	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
X	1	X	X	X	X	X	X	0110
1	X	X	X	0	0	0	0	0010
1	X	X	X	0	0	1	0	0110
1	X	X	X	0	1	0	0	0000
1	X	X	X	0	1	0	1	0001
1	X	X	X	1	0	1	0	0111


FIGURE 5.13 The truth table for the three ALU control bits (called Operation). The inputs are the ALUOp and function code field. Only the entries for which the ALU control is needed are shown. Some don't-care entries have been added. For example, the ALUOp does not use the encoding 11, so the truth table can contain entries 1X and X1, other than 10 and 01. Also, when the function field is used, the first two bits (F5 and F4) of these instructions are always 0X, so they are don't-care terms and are replaced with X's in the truth table.

instr	RegWrite	ALUSrc	MemW	MemRead	MemtoReg	RegSrc
lw	1	1	0	1	1	0
sw	0	1	1	0	X	0
add	1	0	0	0	0	0
sub	1	0	0	0	0	0
slt	1	0	0	0	0	0
or	1	0	0	0	0	0
beq	0	0	0	0	X	0
j	0	0	0	0	X	0

 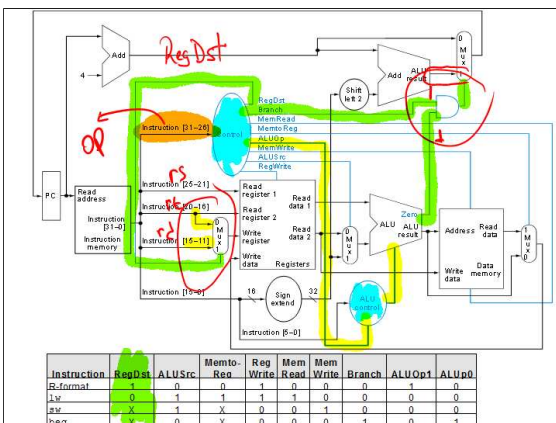

Control

 
- Simple combinational logic (truth tables)



©2004 Morgan Kaufmann Publishers, Inc. 21

Our Simple Control Structure

 - All of the logic is combinational
- We wait for everything to settle down, and the right thing to be done
 - ALU might not produce "right answer" right away
 - we use write signals along with clock to determine when to write
- Cycle time determined by length of the longest path




We are ignoring some details like setup and hold times

©2004 Morgan Kaufmann Publishers, Inc. 22

Single Cycle Implementation

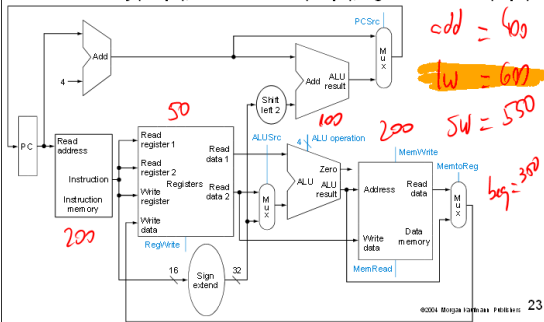
- Calculate cycle time assuming negligible delays except:
 - memory (200ps), ALU and adders (100ps), register file access (50ps)



©2004 Morgan Kaufmann Publishers, Inc. 23

Where we are headed

 - Single Cycle Problems:
 - what if we had a more complicated instruction like floating point?
 - wasteful of area
- One Solution:
 - use a "smaller" cycle time
 - have different instructions take different numbers of cycles
 - a "multicycle" datapath:



©2004 Morgan Kaufmann Publishers, Inc. 24

Multicycle Approach

- We will be reusing functional units
 - ALU used to compute address and to increment PC
 - Memory used for instruction and data
- Our control signals will not be determined directly by instruction
 - e.g., what should the ALU do for a "subtract" instruction?
- We'll use a finite state machine for control


©2004 Morgan Kaufmann Publishers, Inc. 25

Multicycle Approach

- Break up the instructions into steps, each step takes a cycle
 - balance the amount of work to be done
 - restrict each cycle to use only one major functional unit
- At the end of a cycle
 - store values for use in later cycles (easiest thing to do)
 - introduce additional "internal" registers

©2004 Morgan Kaufmann Publishers, Inc. 26

Multicycle Approach

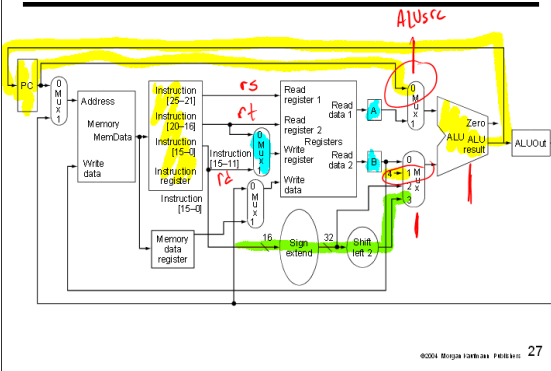

Instructions from ISA perspective

- Consider each instruction from perspective of ISA.
 - Example:
 - The add instruction changes a register.
 - Register specified by bits 15:11 of instruction.
 - New value is the sum ("op") of two registers.
 - Registers specified by bits 25:21 and 20:16 of the instruction
- $$\text{Reg}[\text{Memory}[\text{PC}][15:11]] \leftarrow \text{Reg}[\text{Memory}[\text{PC}][25:21]] \text{ op } \text{Reg}[\text{Memory}[\text{PC}][20:16]]$$
- In order to accomplish this we must break up the instruction. (kind of like introducing variables when programming)

Breaking down an instruction

- ISA definition of arithmetic:

$$\text{Reg}[\text{Memory}[\text{PC}][15:11]] \leftarrow \text{Reg}[\text{Memory}[\text{PC}][25:21]] \text{ op } \text{Reg}[\text{Memory}[\text{PC}][20:16]]$$
- Could break down to:
 - $\text{IR} \leftarrow \text{Memory}[\text{PC}]$ (Busca)
 - $A \leftarrow \text{Reg}[\text{IR}[25:21]]$
 - $B \leftarrow \text{Reg}[\text{IR}[20:16]]$
 - $\text{ALUOut} \leftarrow A \text{ op } B$ (Execution)
 - $\text{Reg}[\text{IR}[15:11]] \leftarrow \text{ALUOut}$ (A op B)
- We forgot an important part of the definition of arithmetic!
 - $\text{PC} \leftarrow \text{PC} + 4$

Idea behind multicycle approach

- We define each instruction from the ISA perspective (do this!)
- Break it down into steps following our rule that data flows through at most one major functional unit (e.g., balance work across steps)
- Introduce new registers as needed (e.g. A, B, ALUOut, MDR, etc.)
- Finally try and pack as much work into each step (avoid unnecessary cycles) while also trying to share steps where possible (minimizes control, helps to simplify solution)
- Result: Our book's multicycle implementation!

Five Execution Steps

- Instruction Fetch (Busca)
- Instruction Decode and Register Fetch (Generics)
- Execution, Memory Address Computation, or Branch Completion
- Memory Access or R-type instruction completion
- Write-back step

INSTRUCTIONS TAKE FROM 3-5 CYCLES!

Step 1: Instruction Fetch

- Use PC to get instruction and put it in the Instruction Register.
- Increment the PC by 4 and put the result back in the PC.
- Can be described succinctly using RTL "Register-Transfer Language"

$\text{IR} \leftarrow \text{Memory}[\text{PC}]$
 $\text{PC} \leftarrow \text{PC} + 4$

Can we figure out the values of the control signals?

What is the advantage of updating the PC now?

Step 2: Instruction Decode and Register Fetch

- Read registers *rs* and *rt* in case we need them
- Compute the branch address in case the instruction is a branch
- RTL:

$A \leftarrow \text{Reg}[\text{IR}[25:21]]$; *rs*
 $B \leftarrow \text{Reg}[\text{IR}[20:16]]$; *rt*
 $\text{ALUOut} \leftarrow \text{PC} + (\text{sign-extend}(\text{IR}[15:0]) \ll 2)$; *imm*

- We aren't setting any control lines based on the instruction type (we are busy "decoding" it in our control logic)

$$\left(\frac{\text{PC} + 4}{\text{PC}} \right) + \text{imm} \ll 2$$

Step 3 (instruction dependent)

- ALU is performing one of three functions, based on instruction type

- Memory Reference: *lw/sw*

$\text{ALUOut} \leftarrow A + \text{sign-extend}(\text{IR}[15:0])$

- R-type: *add, sub, slt*

$\text{ALUOut} \leftarrow A \text{ op } B$

- Branch: *beg*

$\text{if } (A=B) \text{ PC} \leftarrow \text{ALUOut}$

Step 4 (R-type or memory-access)

- Loads and stores access memory

$\text{MDR} \leftarrow \text{Memory}[\text{ALUOut}]$; *lw*
 or
 $\text{Memory}[\text{ALUOut}] \leftarrow B$; *sw*

- R-type instructions finish

$\text{Reg}[\text{IR}[15:11]] \leftarrow \text{ALUOut}$

The write actually takes place at the end of the cycle on the edge

Write-back step

- $\text{Reg}[\text{IR}[20:16]] \leftarrow \text{MDR}$

Which instruction needs this?

lw

Summary:

Step name	R-type instructions	Memory-reference instructions	Branches	Jumps
Instruction fetch	$\text{PC} \leftarrow \text{PC} + 4$	$\text{PC} \leftarrow \text{Memory}[\text{PC}]$	$\text{PC} \leftarrow \text{PC} + 4$	$\text{PC} \leftarrow \text{PC} + 4$
Instruction decode/register fetch	$A \leftarrow \text{Reg}[\text{IR}[25:21]]$ $B \leftarrow \text{Reg}[\text{IR}[20:16]]$	$A \leftarrow \text{Reg}[\text{IR}[25:21]]$ $B \leftarrow \text{Reg}[\text{IR}[20:16]]$	$A \leftarrow \text{Reg}[\text{IR}[25:21]]$ $B \leftarrow \text{Reg}[\text{IR}[20:16]]$	$A \leftarrow \text{Reg}[\text{IR}[25:21]]$ $B \leftarrow \text{Reg}[\text{IR}[20:16]]$
Execution, address computation, branch/jump completion	$\text{ALUOut} \leftarrow A \text{ op } B$	$\text{ALUOut} \leftarrow A + \text{sign-extend}(\text{IR}[15:0])$	$\text{if } (A=B) \text{ PC} \leftarrow \text{ALUOut}$	$\text{PC} \leftarrow \text{PC}[\text{31:28}], \text{IR}[\text{25:0}] \ll 2$
Memory access or register file completion	$\text{Reg}[\text{IR}[15:11]] \leftarrow \text{ALUOut}$	Load: $\text{MDR} \leftarrow \text{Memory}[\text{ALUOut}]$ Store: $\text{Memory}[\text{ALUOut}] \leftarrow B$		
Memory read completion		Load: $\text{Reg}[\text{IR}[20:16]] \leftarrow \text{MDR}$		

FIGURE 5.30 Summary of the steps taken to execute any instruction class. Instructions take from three to five execution steps. The first two steps are independent of the instruction class. After these steps, an instruction takes from one to three more cycles to complete, depending on the instruction class. The empty entries for the Memory access step or the Memory read completion step indicate that the particular instruction class takes fewer cycles. In a multipipeline implementation, a new instruction will be started as soon as the current instruction completes, so these cycles are not idle or wasted. As mentioned earlier, the register file actually reads every cycle, but as long as the IR does not change, the values read from the register file are identical. In particular, the value read into register B during the Instruction decode stage, for a branch or R-type instruction, is the same as the value stored into B during the Execution stage and then used in the Memory access stage for a store word instruction.

Simple Questions

- How many cycles will it take to execute this code?

21

```






5 lw $t2, 0($t3)
5 lw $t3, 4($t3)
3 beg $t2, $t3, Label
3 add $t5, $t2, $t3
4 sw $t5, 8($t3)
Label:
...

```
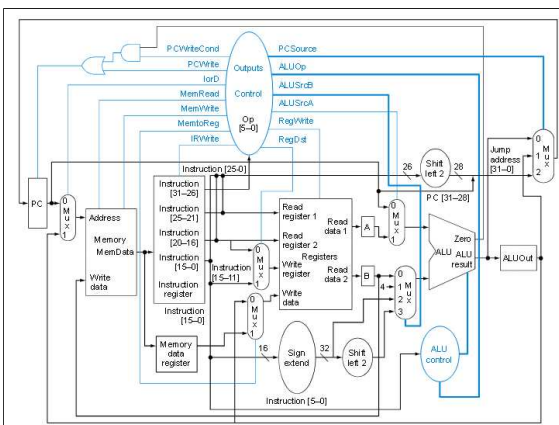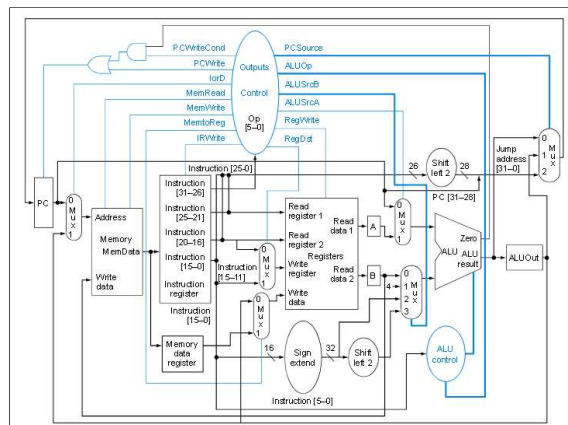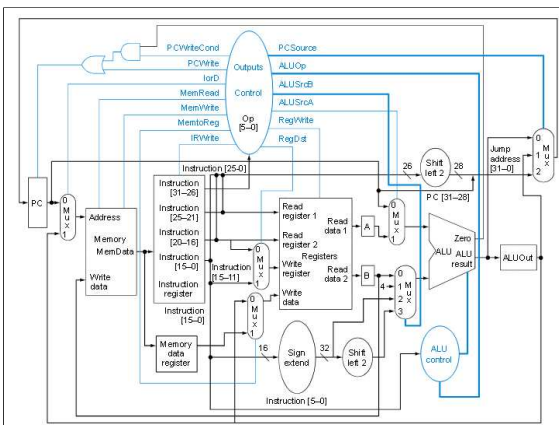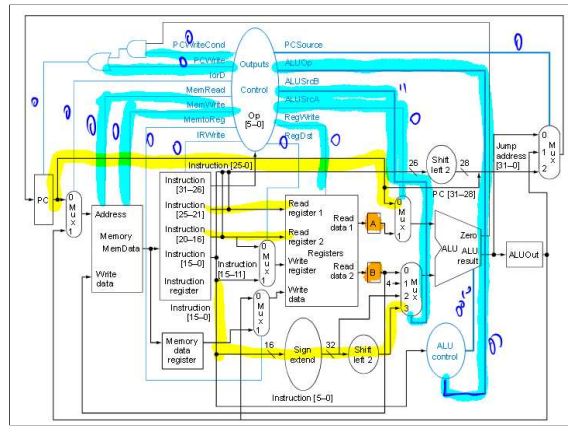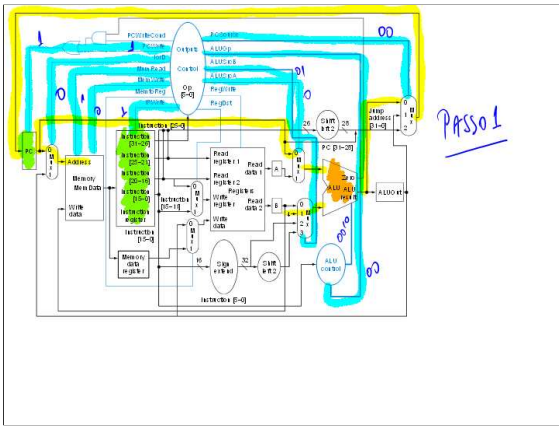
#assume not


- What is going on during the 8th cycle of execution?
- In what cycle does the actual addition of \$t2 and \$t3 takes place?





Review: finite state machines

 - **Finite state machines:**
 - a set of states and
 - next state function (determined by current state and the input)
 - output function (determined by current state and possibly input)




- We'll use a Moore machine (output based only on current state)

Implementing the Control

- Value of control signals is dependent upon:
 - what instruction is being executed
 - which step is being performed
- Use the information we've accumulated to specify a finite state machine
 - specify the finite state machine graphically, or
 - use microprogramming
- Implementation can be derived from specification


Graphical Specification of FSM

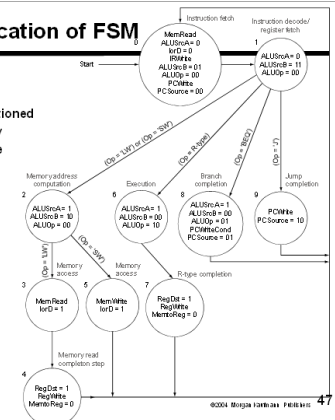- Note:
 - don't care if not mentioned
 - asserted if name only
 - otherwise exact value
- How many state bits will we need?




Finite State Machine for Control

- Implementation:

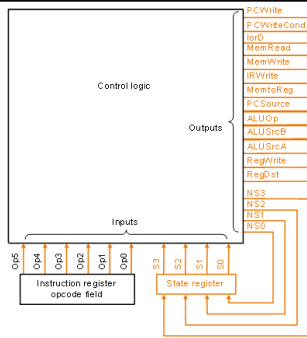


PLA Implementation

 - If I picked a horizontal or vertical line could you explain it?



ROM Implementation

 - ROM = "Read Only Memory"
 - values of memory locations are fixed ahead of time
- A ROM can be used to implement a truth table
 - if the address is m-bits, we can address 2^m entries in the ROM.
 - our outputs are the bits of data that the address points to.



m is the "height", and n is the "width"

ROM Implementation


- How many inputs are there?
 - 6 bits for opcode, 4 bits for state = 10 address lines (i.e., $2^{10} = 1024$ different addresses)
- How many outputs are there?
 - 16 datapath-control outputs, 4 state bits = 20 outputs
- ROM is $2^{10} \times 20 = 20K$ bits (and a rather unusual size)
- Rather wasteful, since for lots of the entries, the outputs are the same
 - i.e., opcode is often ignored

ROM vs PLA


- Break up the table into two parts
 - 4 state bits tell you the 16 outputs, $2^4 \times 16$ bits of ROM
 - 10 bits tell you the 4 next state bits, $2^{10} \times 4$ bits of ROM
 - Total: 4.3K bits of ROM
- PLA is much smaller
 - can share product terms
 - only need entries that produce an active output
 - can take into account don't cares
- Size is $(\#inputs \times \#product\text{-terms}) + (\#outputs \times \#product\text{-terms})$
For this example = $(10 \times 17) + (20 \times 17) = 510$ PLA cells
- PLA cells usually about the size of a ROM cell (slightly bigger)

Another Implementation Style

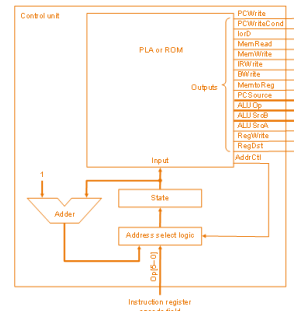
- Complex instructions: the "next state" is often current state + 1



Details

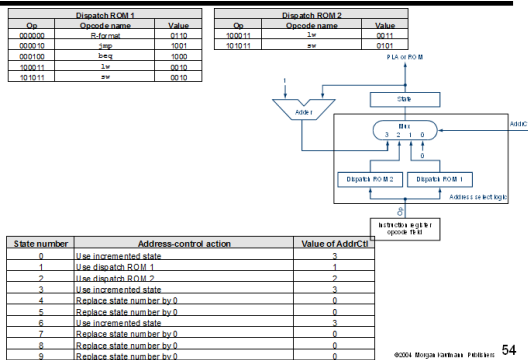

Microprogramming

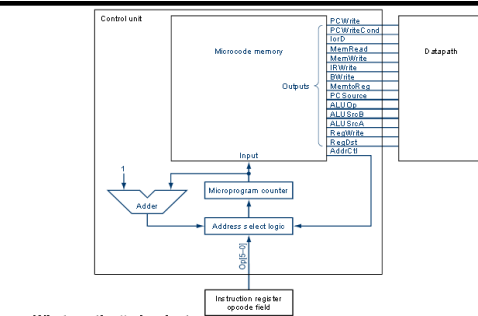

- What are the "microinstructions"?

Microprogramming

- A specification methodology
 - appropriate if hundreds of opcodes, modes, cycles, etc.
 - signals specified symbolically using microinstructions

Label	ALU control	SRC1	SRC2	Register control	Memory	PCWrite control	Sequencing
Fetch	Add	PC	4		Read PC	ALU	Seq
	Add	PC	ExtShift	Read			Dispatch 1
Mem1	Add	A	Extend		Read ALU		Dispatch 2
LW2				Write MDR			Seq
SW2				Write ALU			Fetch
Rformat1	Func code	A	B	Write ALU			Seq
BEQ1	Subtl	A	B		ALUOut-cond		Fetch
JUMP1					Jump address		Fetch

- Will two implementations of the same architecture have the same microcode?
- What would a microassembler do?

Microinstruction format

Field name	Value	Signal's active	Comment
ALU control	ADD	ALUOp = 00	Cause the ALU to add
	SUB	ALUOp = 01	Cause the ALU to subtract; this implements the compare for branches
SRC1	Func code	ALUSrcA = 10	Use the instruction's function code to determine the ALU source
	PC	ALUSrcA = 0	Use the PC as the first ALU input
SRC2	A	ALUSrcB = 1	Register A is the first ALU input
	B	ALUSrcB = 00	Register B is the second ALU input
	s	ALUSrcB = 01	Use s as the second ALU input
	Extend	ALUSrcB = 10	Use output of the sign extension unit as the second ALU input
Register control	Read	ALUSrcB = 11	Use the output of the sign extension unit as the second ALU input
	Write ALU	RegWrite, RegDst = 1, MemWrtEq = 0	Write a register using the r field of the IR as the register number and the contents of the ALUOut as the data
Memory	Write MDR	RegWrite, RegDst = 0, MemWrtEq = 1	Write a register using the r field of the IR as the register number and the contents of the MDR as the data
	Read PC	MemRead, ALUSrcA = 1	Read memory using the PC as address; write result into IR (and the MDR)
PC write control	Read ALU	MemRead, ALUSrcA = 1	Read memory using the ALUOut as address; write result into MDR
	Write ALU	MemWrite, ALUSrcA = 1, ALUSrcB = 0	Write memory using the ALUOut as address; contents of B as the data
Sequencing	ALU	PCSource = 00	Write the output of the ALU into the PC
	ALUOut-cond	PCSource = 01	If the Zero output of the ALU is active, write the PC with the contents of the register ALUOut
Sequencing	Jump address	PCSource = 10, PCWrite = 1	Write the PC with the jump address from the instruction
	Seq	AddrCtrl = 11	Choose the next microinstruction sequentially
Sequencing	Fetch	AddrCtrl = 00	Go to the first microinstruction to begin a new instruction
	Dispatch 1	AddrCtrl = 01	Dispatch using the ROM 1
	Dispatch 2	AddrCtrl = 10	Dispatch using the ROM 2

Maximally vs. Minimally Encoded

- No encoding:
 - 1 bit for each datapath operation
 - faster, requires more memory (logic)
 - used for Vax 780 — an astonishing 400K of memory!
- Lots of encoding:
 - send the microinstructions through logic to get control signals
 - uses less memory, slower
- Historical context of CISC:
 - Too much logic to put on a single chip with everything else
 - Use a ROM (or even RAM) to hold the microcode
 - It's easy to add new instructions

Microcode: Trade-offs

- Distinction between specification and implementation is sometimes blurred
- Specification Advantages:
 - Easy to design and write
 - Design architecture and microcode in parallel
- Implementation (off-chip ROM) Advantages
 - Easy to change since values are in memory
 - Can emulate other architectures
 - Can make use of internal registers
- Implementation Disadvantages. SLOWER now that:
 - Control is implemented on same chip as processor
 - ROM is no longer faster than RAM
 - No need to go back and make changes


Chapter 5 Summary

- If we understand the instructions...
 - We can build a simple processor!
- If instructions take different amounts of time, multi-cycle is better
- Datapath implemented using:
 - Combinational logic for arithmetic
 - State holding elements to remember bits
- Control implemented using:
 - Combinational logic for single-cycle implementation
 - Finite state machine for multi-cycle implementation

Exceptions (MIPS)

- **Exception:** An unscheduled event that disrupts program execution
- **Interrupt:** An exception that comes from outside of the processor
- **New Registers:** EPC and Cause
- **Two Methods:** Simple and Vektored

Datapath

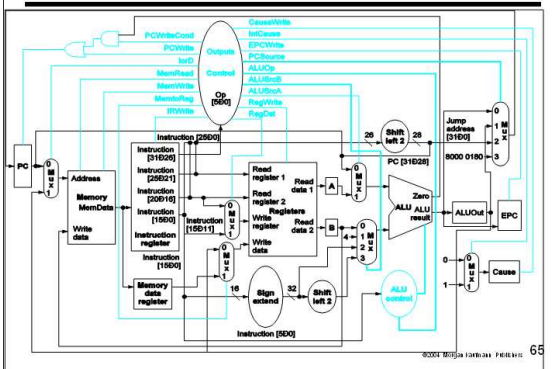

Control

